

New preamplifier
in TSMC130nm
for the ATLAS
LArg Electromagnetic
Calorimeter upgrade





Gisele Martin-Chassard

Upgrade motivations for front-end readout

- Speed up the digitization up to 40MHz
- Decrease power dissipation by 10
→ Gather all blocks in an ASIC

Cornerstone = Preamplifier :
“Universal” preamplifier with
selectable dynamic range
and input impedance (25/50
Ohm)

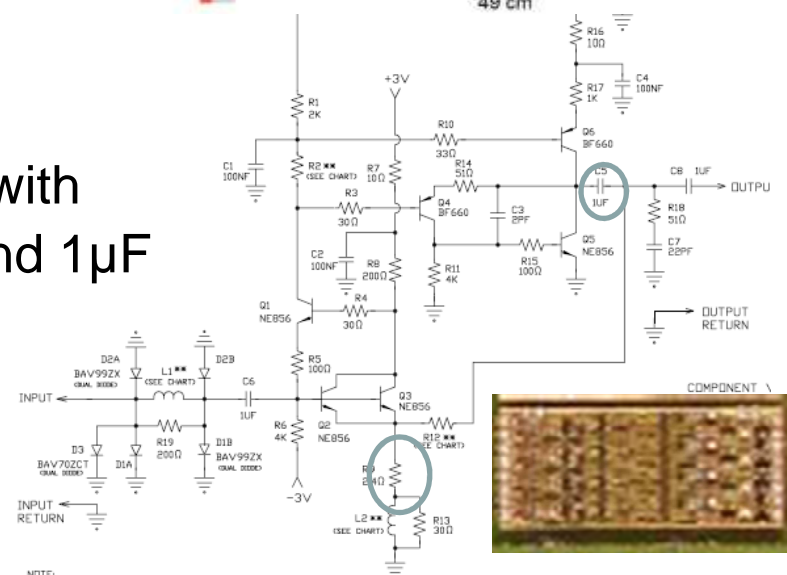 Preamp : 0T configuration with
discrete components such as 2.4 Ω and 1 μF
⇒ difficult to integrate in an ASIC
⇒ New design



- Precise Input impedance Z_{in} 50 Ω (Front) or 25 Ω (Middle/Back) to terminate the cables from the detector
- Low noise < 10 Ω , with C_d 400 pF (Front) or 1 nF (Middle/Back) and $t_p=50$ ns
- ENI as low as possible (large C_d , long duration signal) :
0T50 400pF: ENI@50ns=55nA, 0T25 1.5nF: ENI@50ns=150 nA
- Dynamic range:
 - Input current 10 μ A up to 2 mA (Front)
 - Input current 10 μ A up to 10 mA (Middle/Back)
- Radiation resistance

New line-terminating preamp

- New « negative noise figure preamp » (patent filed)

- Preamp Input impedance
 - Super Common Base: low input impedance
 - Amplifier = low noise voltage sensitive
 - Fine tuning of Z_{in} ($\pm 5\%$) possible with C_2

$$Z_{in}^{PA} = \frac{R_0 + Z_{in}(SCB)}{1 + |G|}$$

- Noise

- Electronically cooled resistor

$$\frac{4kTR_0}{(1 + |G|)^2}$$

- Preamp 50 Ω , 10 μ A to 2 mA max, $C_d=400$ pF


- Z_{in} tuning: $R_0= 500 \Omega$, $G = -C_1/C_2=-9$
- Noise : 5 Ω
- HG dynamic range: $R_f=5$ K (or 10K)

- Preamp 25 Ω , up to 10 mA max, $C_d=1.4$ nF


- $R_0= 100 \Omega$, $G = -C_1/C_2 = -3$
- Noise : 6 Ω
- HG dynamic range: $R_f=1$ K (or 2K)

- HG and LG outputs available :

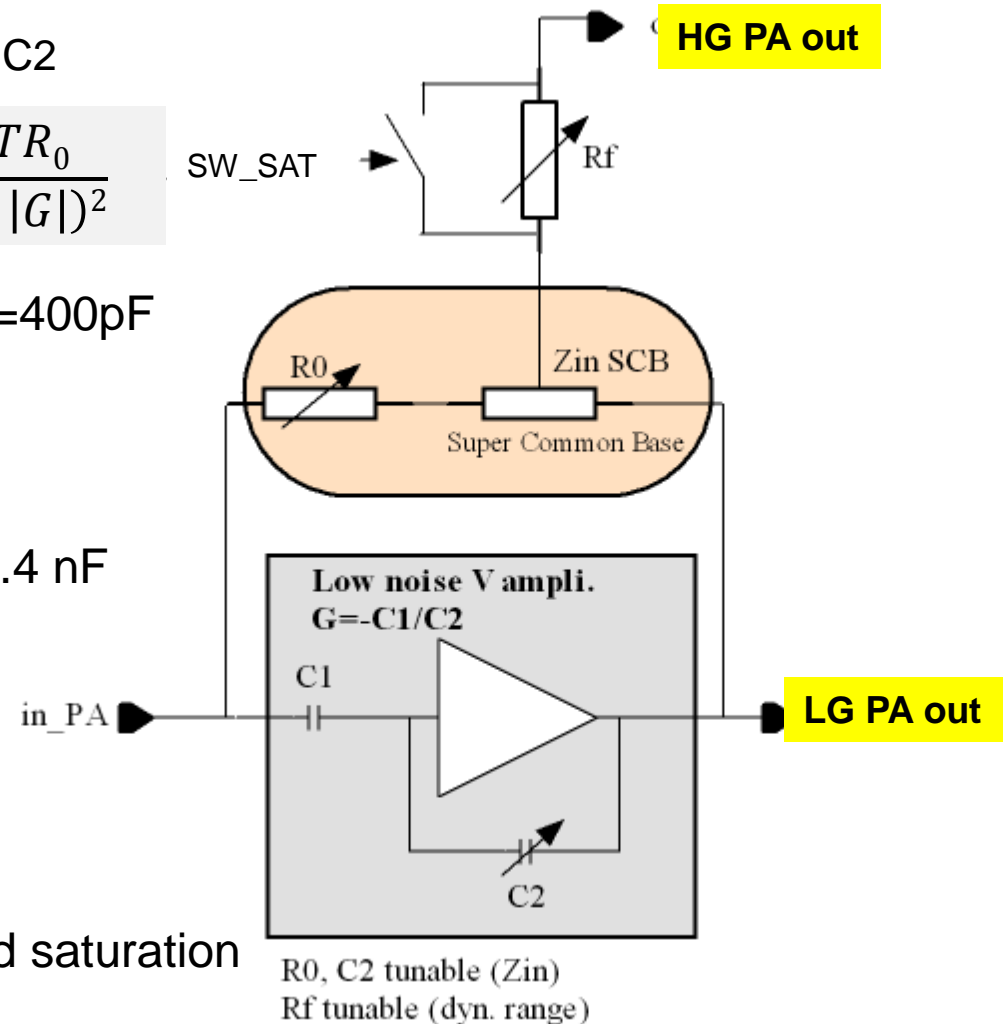
Switch (SW_SAT) to short R_f and to avoid saturation



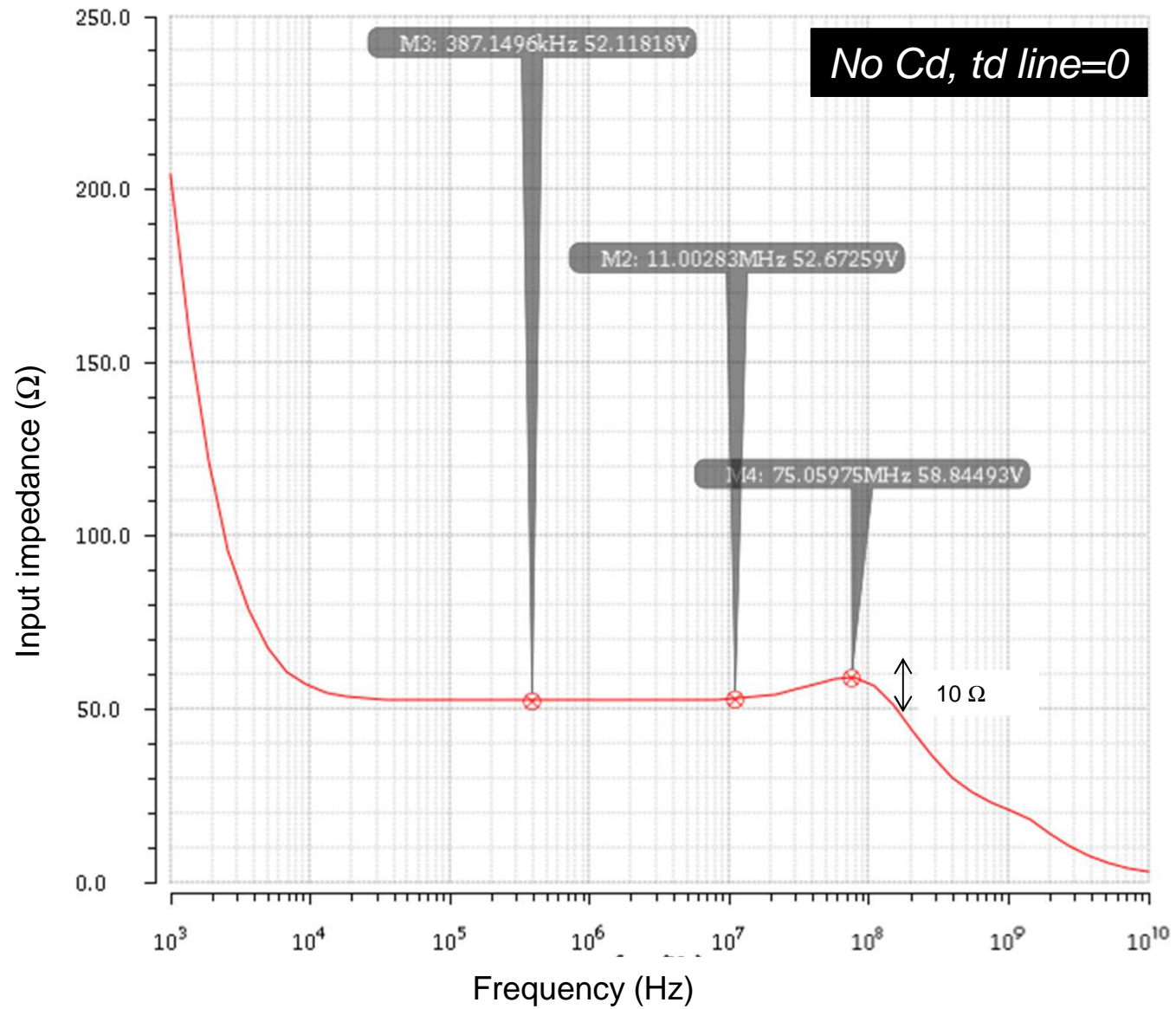
Simulation results: Zin (50 PA) vs frequency




 
Simulation results: 50 Ω HG CRRC² Linearity



 Simulation results: 50 Ω LG CRRC² Linearity



 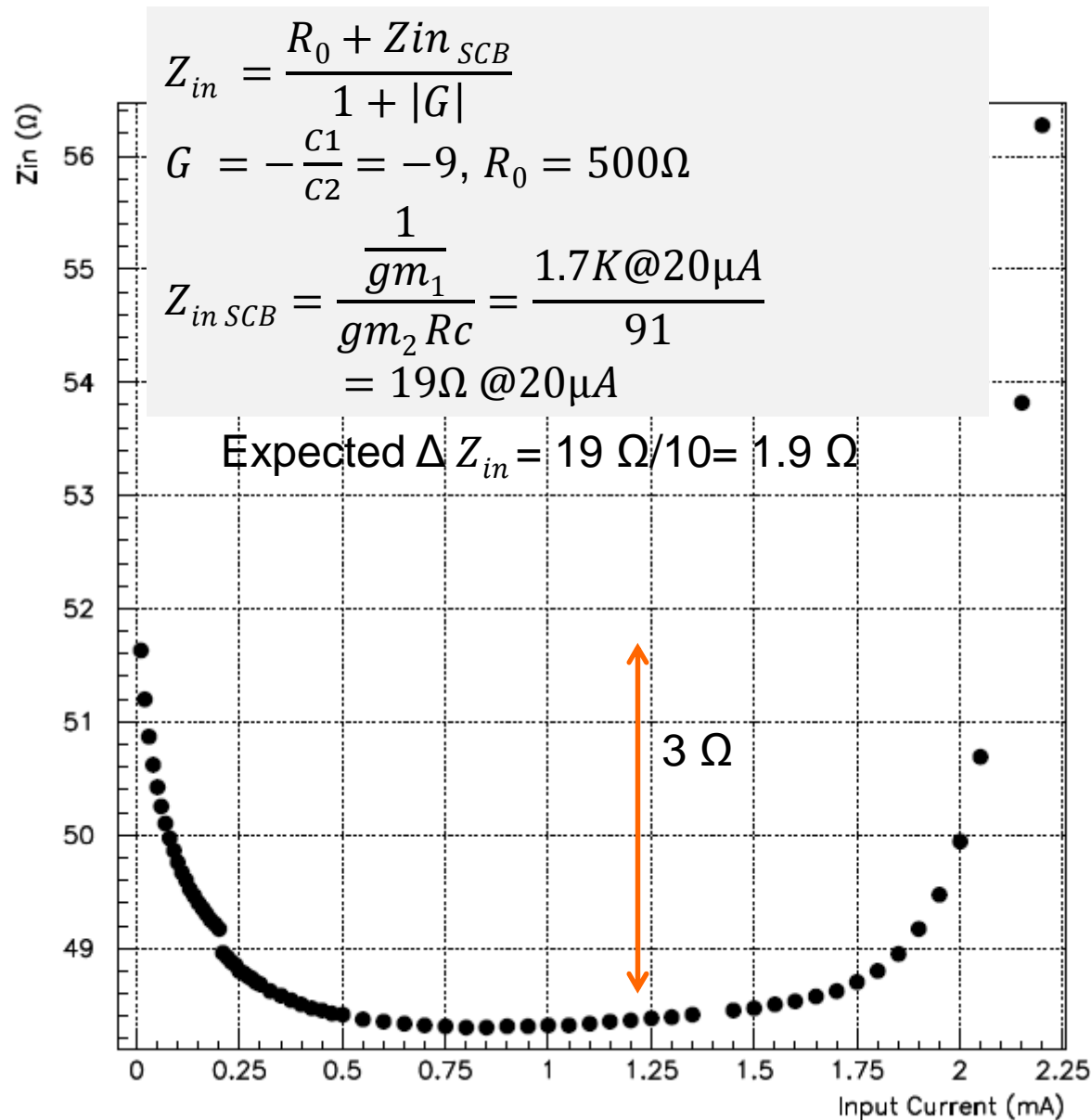
Simulation results: Z_{in} 50 Ω PA vs Input current



Simulation results: HG 50Ω PA Noise



out_HG_PA
Cd=400 pF

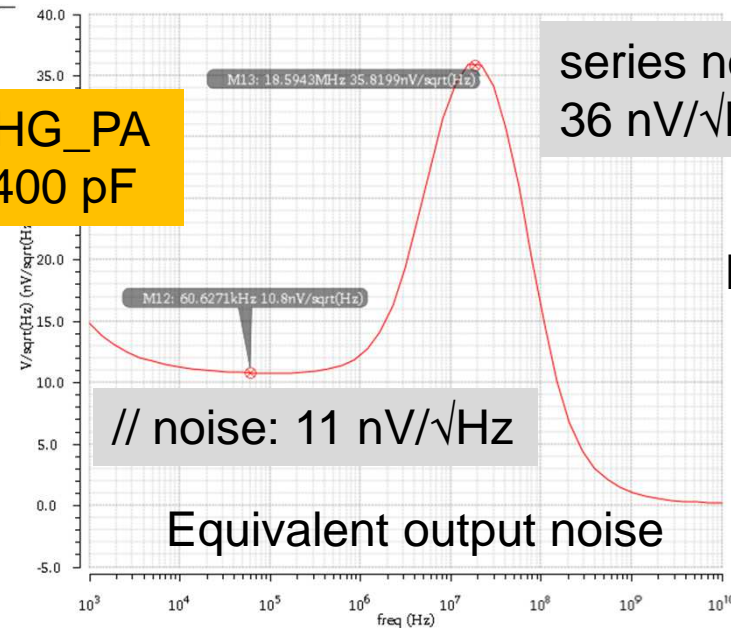

$$\frac{4kTR_0}{(1+|G|)^2} \text{ with } G=-9$$


$R_0=500 \Omega \Rightarrow$ Equ. Noise: 0.28 nV/sqrt(Hz) or 5 Ω

\Rightarrow Voltage gain @ output of the preamp R_f / Z_{in}
 $=5K/50=100$

\Rightarrow Input Noise: 36 nV/100=0.36 nV/sqrt(Hz) or 8 Ω

\Rightarrow **< 10 Ω requirement**

out_CRRC2
 $\tau=15$ ns

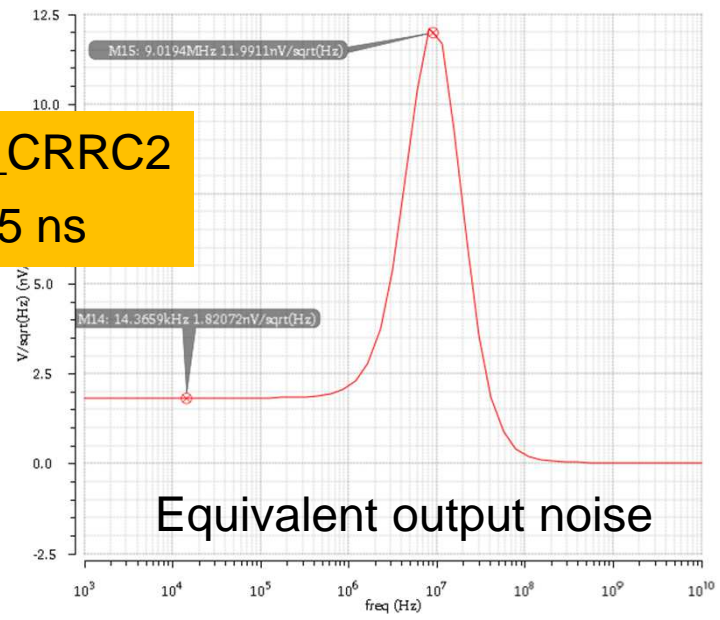

rms noise= 46 μ V


$I_{det}=100 \mu$ A gives 100 mV
at the output of the HG CRRC²

\Rightarrow ENI=46 nA

ENI similar to the ENI measured with the current 0T


0T50 400pF: ENI@50ns=55nA,
0T25 1.5nF: ENI@50ns=150 nA

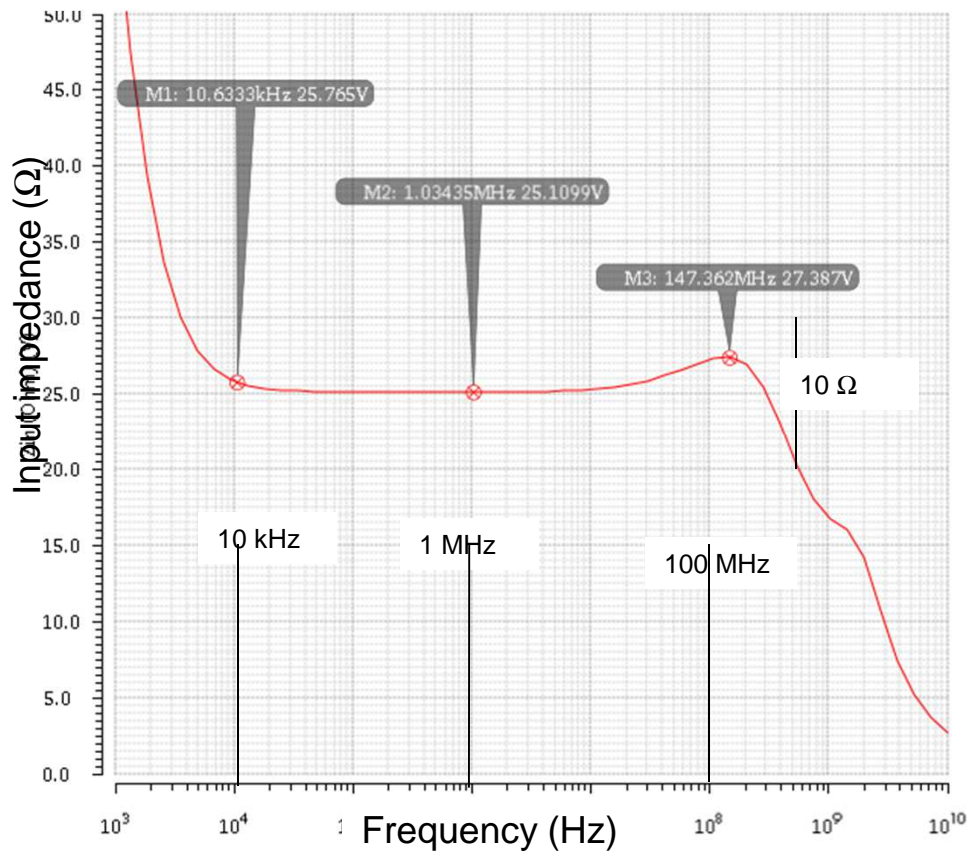Simulation performance results (25 Ω /10 mA)



Impedance flat from 10 kHz to 100 MHz
 < 1 Ω variation versus current due to
 Super Common base Zin variation

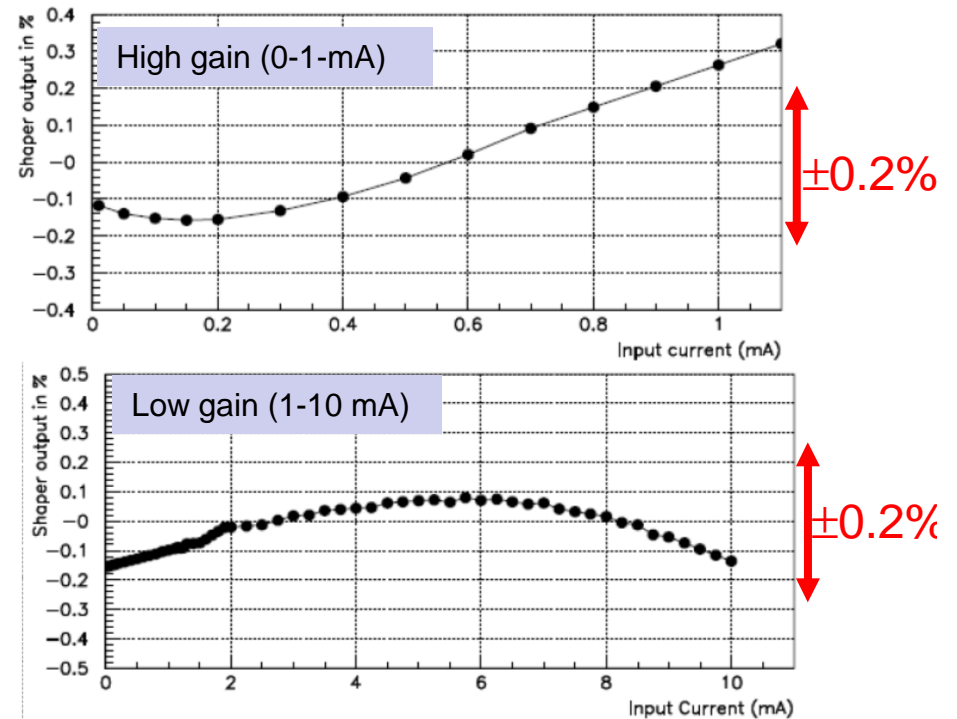Integral non linearity (/linear fit) with CR-RC2 (40 ns peaking time)




Noise dominated by R0 and NMOS
 ampli : 150 nA with 1.5 nF

Chip submitted



8 channels with various preamps :


	Zin	Gain&Dyn range	Others
PA 50A	Fixed Zin (fixed R0 and C2)	Fixed Rf	
PA 50B	Adjustable Zin (with C2)	Adjustable Rf	
PA 25A	Adjustable Zin (with C2)	Adjustable Rf	Input trans area = Nominal size
PA 25B	Adjustable Zin (with C2)	Adjustable Rf	Input trans area = Nominal size/2
PA 25C	Adjustable Zin (with C2)	Adjustable Rf	Input trans area = 2xNominal size
PA 25D	Adjustable Zin (with C2)	Adjustable Rf	protection diodes
PA 25E	Fixed Zin (with C2)	Fixed Rf	
PA 25-50	Switches to choose 25 or 50 Ω Adjustable Zin (with C2 and R0)	Adjustable Rf	

 


Slow Control parameters and switches to change R_0 and C_2 (Zin) and R_f (dyn. Range)
 Each PA can be switched OFF when not used. Outputs (HG and LG) go to pads thru buffer and LG go to discr
 Discr provides antisat signal (1 architecture with 3 various grounding to characterize techno).
 24-bit counter triple voting @ 100MHz to test the digital kit and to simulate digital activity in chip.

Use of 130 nm layout kit has shown to be a bit difficult but chip was submitted on May 15th through CERN/IMEC .




- Collaboration: LAL, OMEGA (+BNL)
 - LAL: N. Morange, L. Serin, S. Simion
 - OMEGA: P. Dinaucourt, C. de La Taille, G. Martin-Chassard, N. Seguin-Moreau
- Integrated preamp
 - 3 designs: OMEGA+LAL (130nm CMOS), BNL (65 nm CMOS) and Penn University (130nm SiGe)
 - Collaborative effort with BNL to converge toward common architecture
- Testbench designed by LAL + BNL
 - Preamps characterization
 - Irradiation tests

 

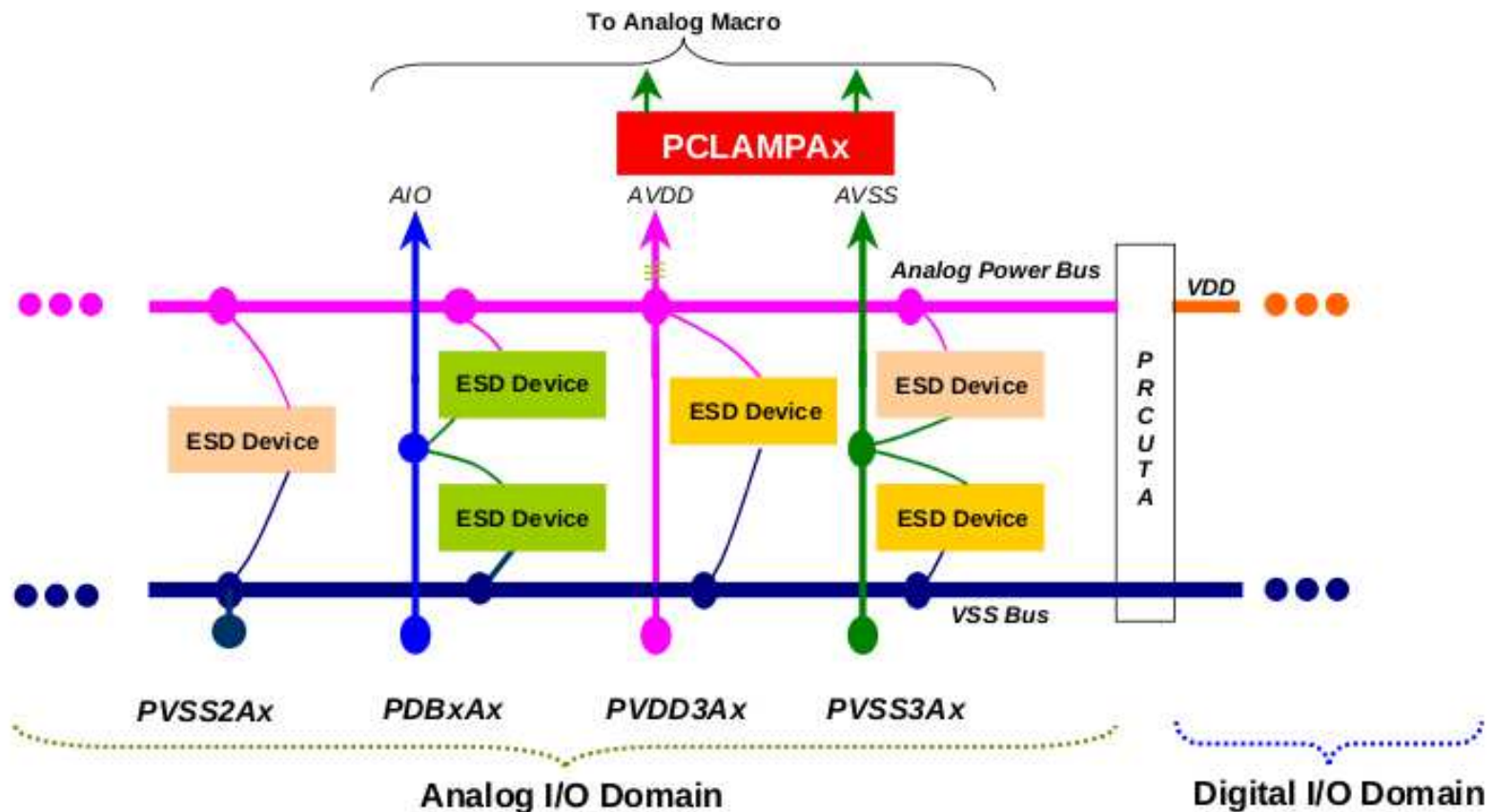
- Pour séparer les masses numériques et analogiques :
PVSS3A non relié au VSS mais nécessite un PCLAMP
- Pour séparer les alim. PRCUTA



Packaging in PGA144 – cavity : 10X10 mm²

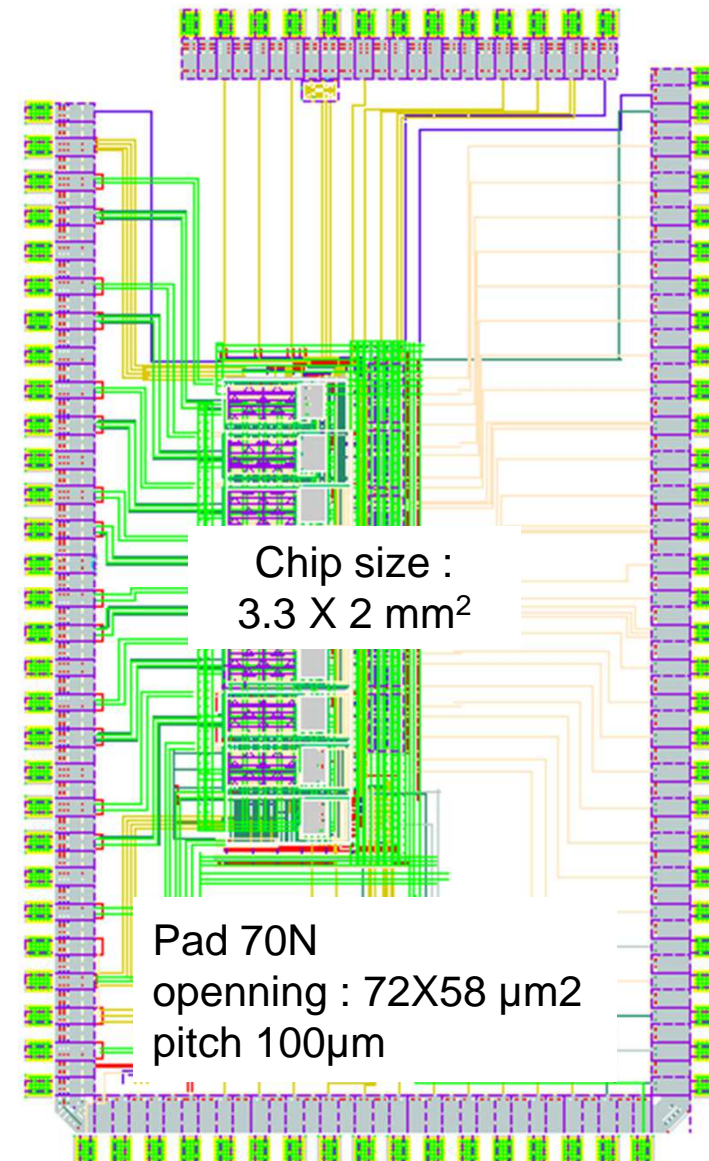  

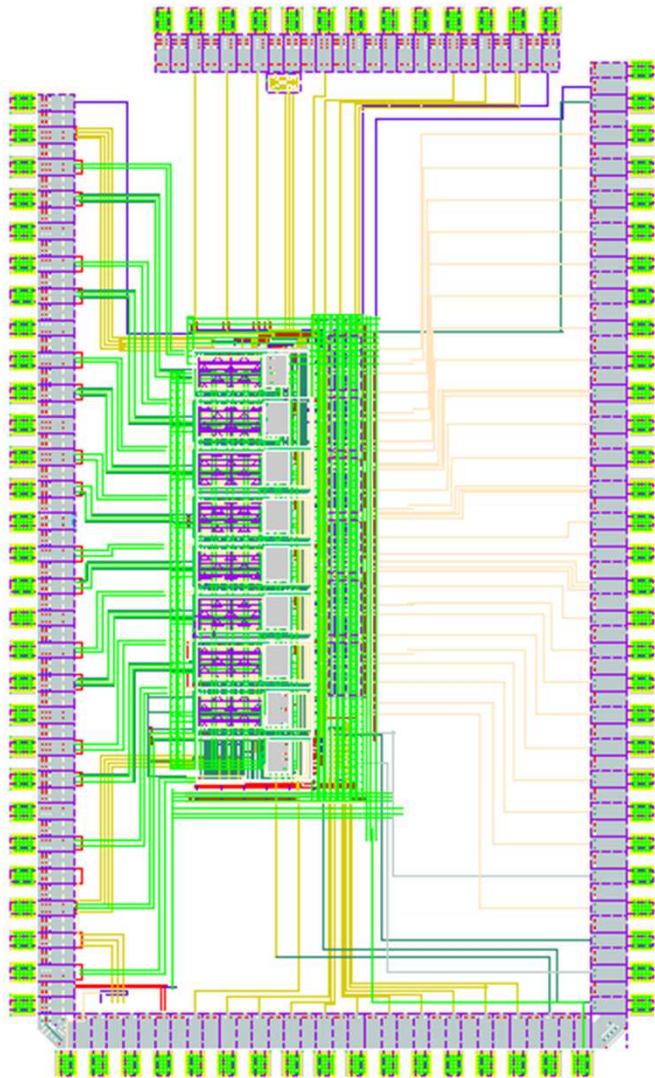Pad 70N + 70G (en quinconces)
opening : 72X58 μm²
pitch 50μm



- Sealring :
- scribeline
 - corners
- Filling :
- diffusion
 - metalx
 - slots

