


OBELIX V1

Digital circuit design

Xu Danwei – CPPM
Maximilian Babeluk -- HEPHY

Content

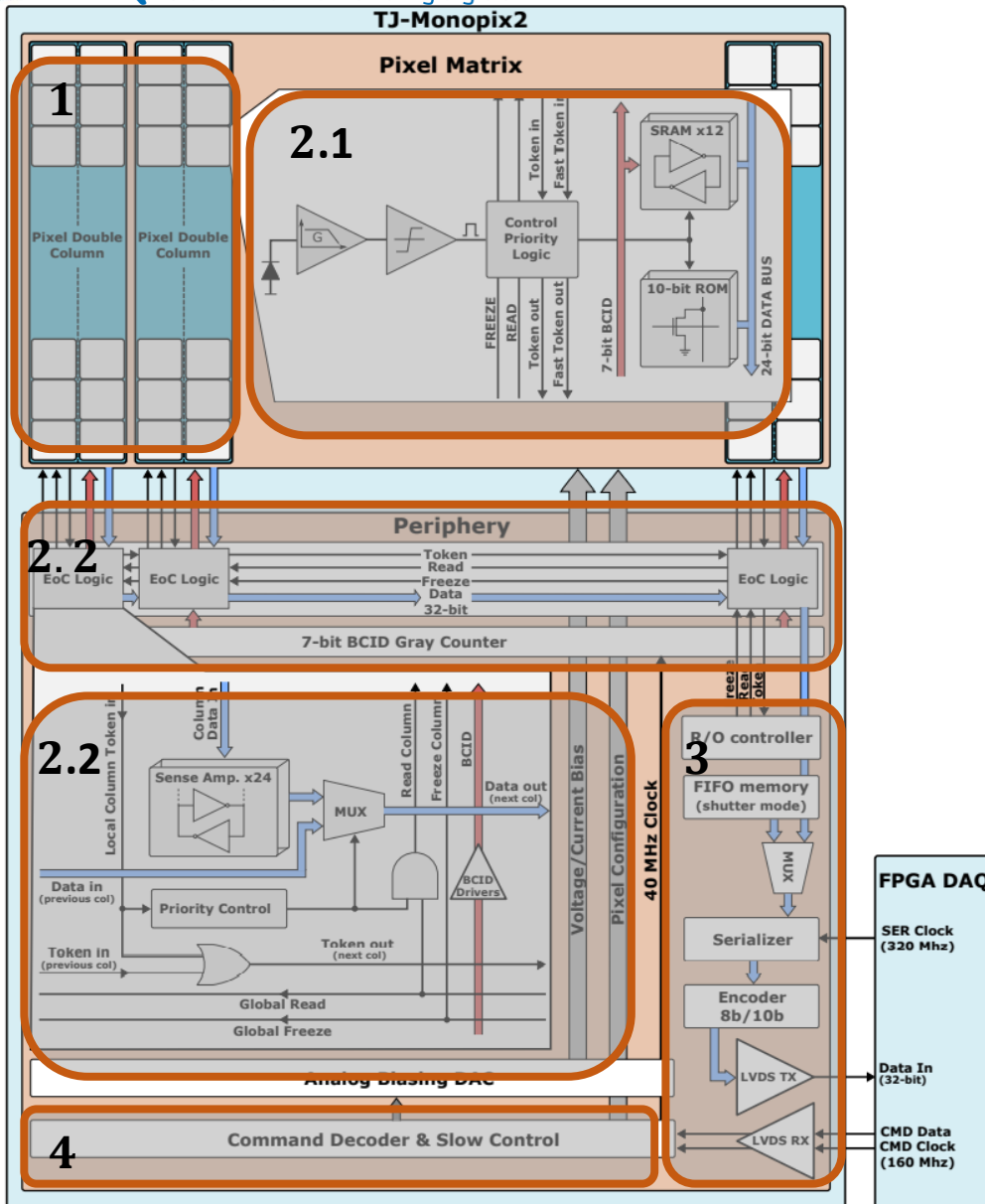- Obelix specifications
- Digital Blocks & description
- Data_path & Clk_path
- Conclusions



- Several parts
 - 1. Pixel matrix – double column
 - 2. Eocs¹ readout logic –
 - 2.1 custom block and data-bus readout circuit
 - 2.2 digital logic, contains a token based priority mechanism
 - 2 modes : direct readout / shutter mode
 - 3. data transmission – transmit output data off-chip
 - 4. command decoder and clk control
-
- Main clk in : 160MHz
 - General function clk : 40MHz;
 - Single output at 320Mb/s;
 - RD53A LHC phase-II upgrade prototype ROIC ;

1: Eoc – End of Column

Figure 1: Architecture of TJ-MONOPIX2

- Main specifications of digital Top
- Main clk in : **160MHz**
- General function clk : from 40MHz to **20 MHz**;
- Single output at **320Mb/s**;
- Area limitation and **power consumption** ;
- **New End-of-column** adapted to Belle II trigger
 - Timestamped hits stored in memories
 - Read-out when timestamps matched with trigger
 - hit rate $\leq 120\text{MHz/cm}^2$
- **RD53B** control protocol from ATLAS CMS;
- TJ 180nm technology

OBELIX functional blocks

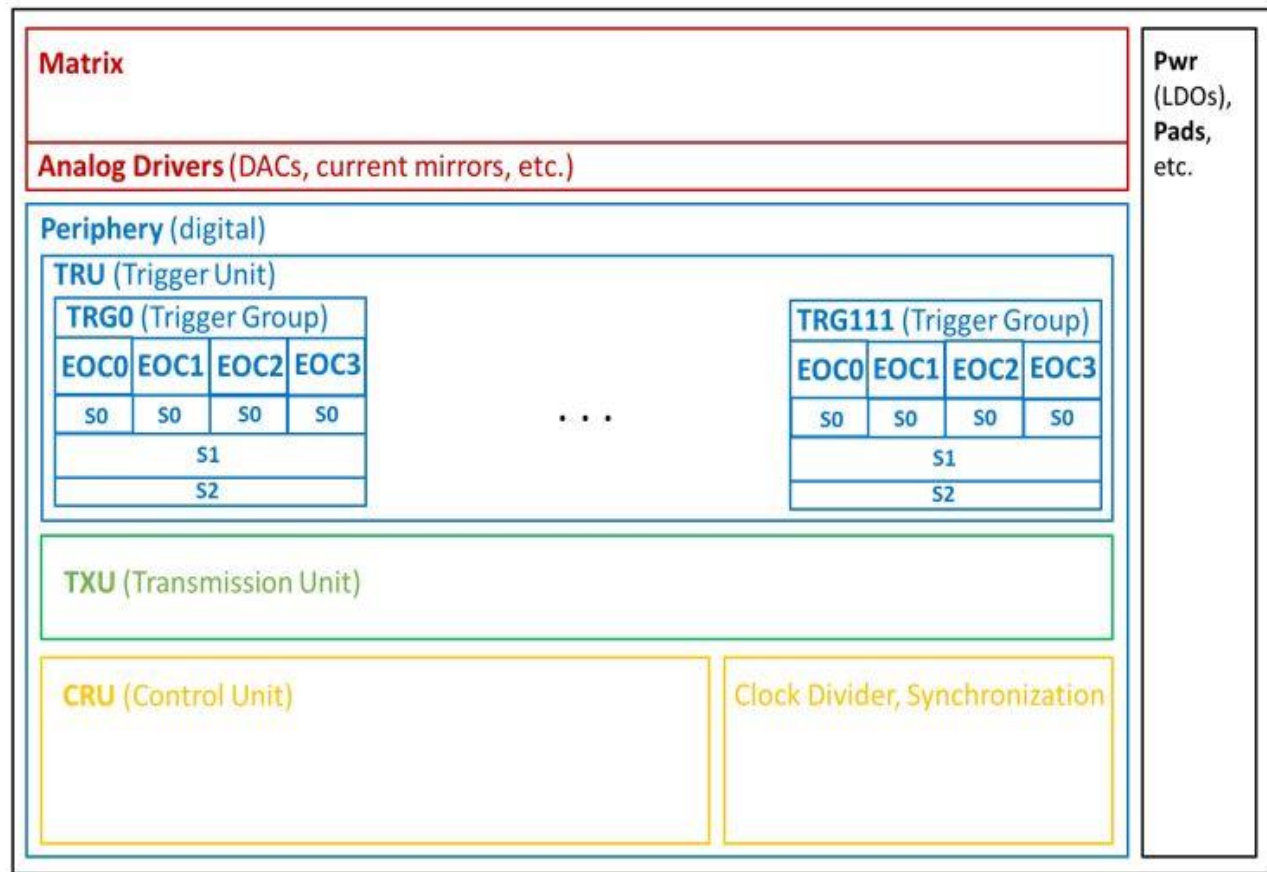


Figure 2 : Functional block of Obelix

RD53B protocol:

<https://cds.cern.ch/record/2665301>

 


Figure 3 : Geometry and overall layout of Obelix

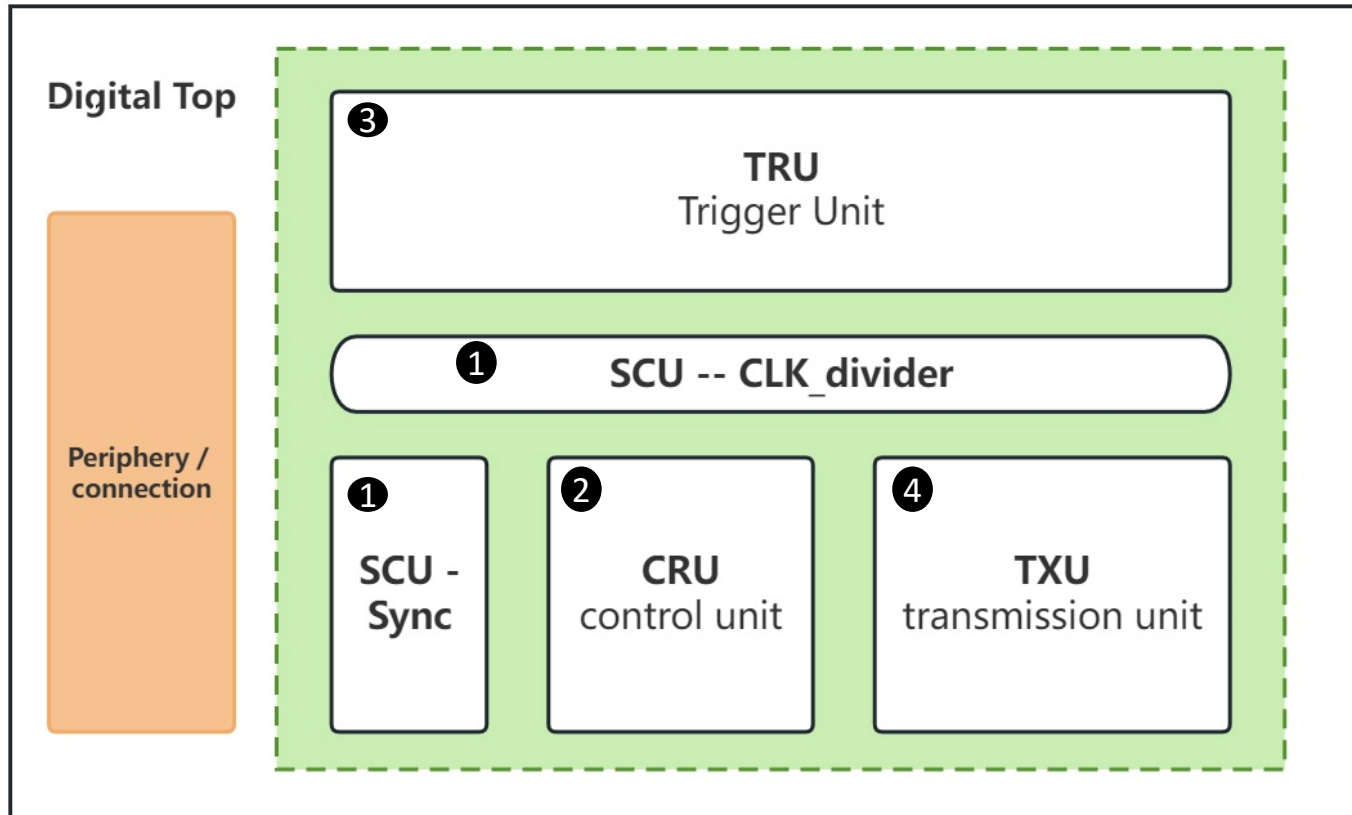


Figure 4 : Module division of Obelix digital top

- Module division : 4 main parts
- **① SCU – sync & clk divider:** digital clk divider, synchronize circuit & clk divider, RxDat format StoP conversion, main function: clock divider, Rx_data SIPO synchronization
- **② CRU – Control Unit:** Implementation RD53B interface, main functions: command decoder, global register configuration
- **③ TRU – Trigger Unit:** Manage pixel data from the matrix-EOC and wait for the trigger to pick them for output
- **④ TXU – TX Unit:** generate output data and sequential output, main functions: data framing, serializer


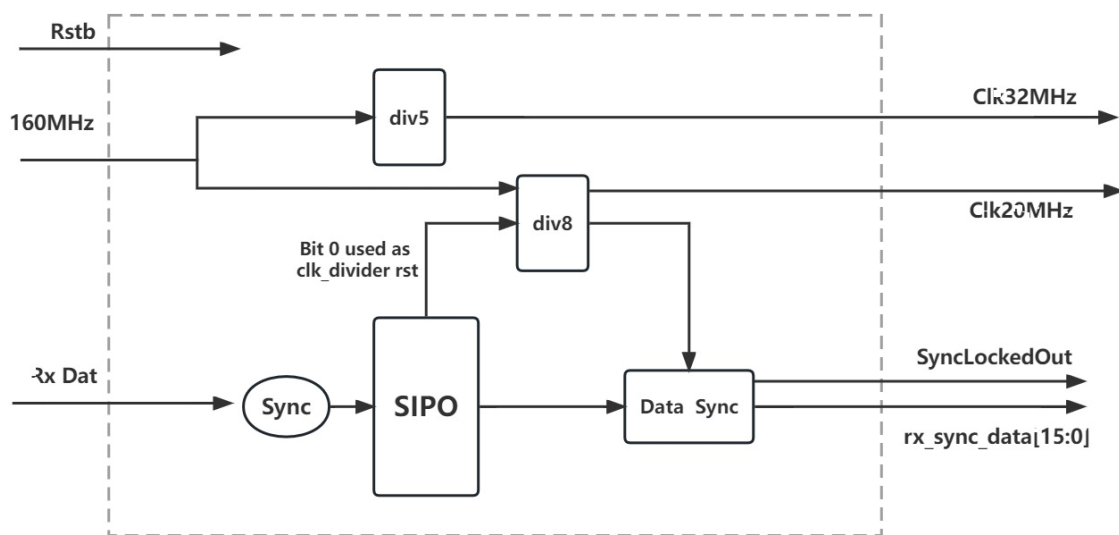


Figure 5 : Structure of SCU

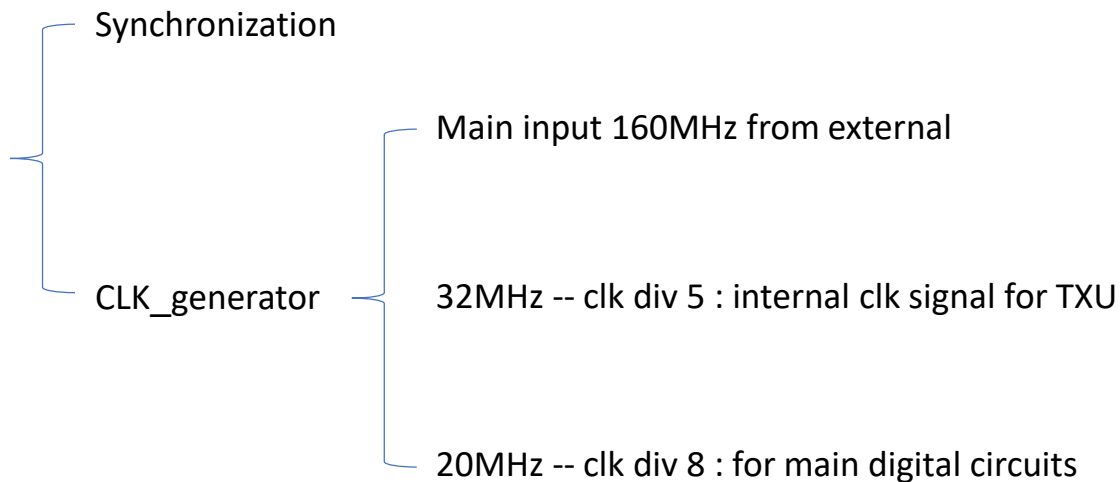


- **SCU**: divider into 2 parts, general specs:
 - Input – clk 160MHz, sync Rstb, RxDat (serial)
 - Output – clk 20MHz, clk 32MHz for other parts, 16-bits RxSyncData(parallel)
- **clk_gene**: clk div modify – div5 & div 8 – counter divider ;
- **Sync**: RxDat SIPO converts – serial string input to 16-bit parallel data output;
 - match keywords 'Sync'
 - data alignment;
 - output 'SyncLockedOut';
 - determine the start point of data;
 - 'Rst' signal generation for 20MHz

Sync [15:0]: '10000001 01111110'

SCU -- CLK Generator & Sync

 - **SCU:**
- Synchronize flow:
- 'Sync' detect ,
- Data alignment ,
- Sync complete
- output 'SyncLockedOut'
- format below



			Comment
serial RxDat received	find 'Sync'		Load data 1 bit a time, and compare with 'Sync', at least 16 clk cycles
	phase_cnt -- 16 bits		
		5 'Sync' detected	
		phase_cnt_last_sync -- lock the phase of first data	phase_cnt_last_sync changes each time a 'Sync' was detect
	generate int_locked		That means the data after the fifth 'Sync' must be the first meaningful data
		after 64 commands received without 'Sync', link loss	
			must send 'Sync' periodically
	if phase_cnt not match for the 'Sync' after the 4th, link loss		

Figure 6 : Synchronization flow

*Case of 'Lock_Loss'
 -- 64 bytes Rx data without 'Sync'
 -- phase not match between two 'Sync'

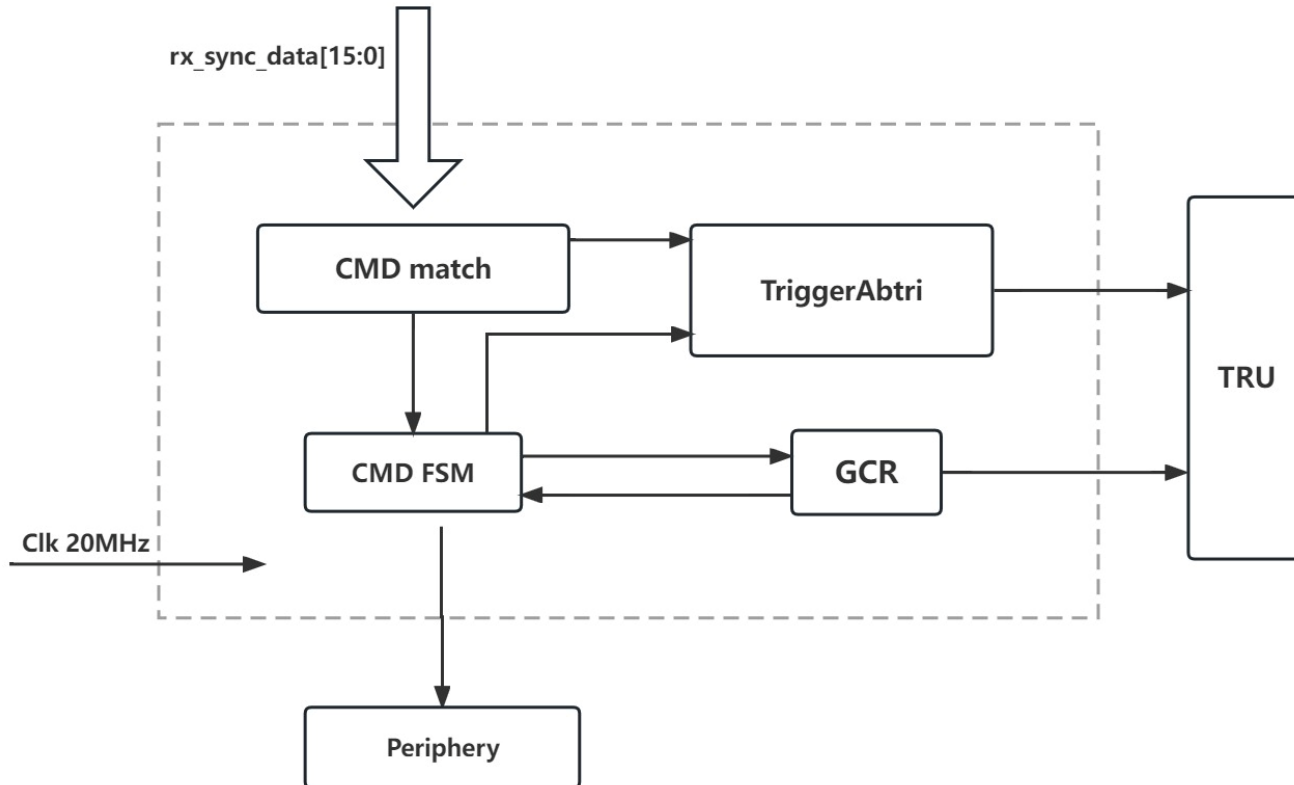


Figure 7 : Structure of CRU

- **CRU**: Use RD53B control protocol from ATLAS CMS;
- **CMD**: almost kept, decoder all the instructions from RxDat to deliver all the commands to other parts of the chip. Most important – **verify the handshake for trigger** between control and chipbottom.
- **GCR**: after collecting all the infos, decide whether to increase or change the default/set register values
- [doc/registers.md · main · VTXUpgrade / obelix1 · GitLab \(desy.de\)](#)

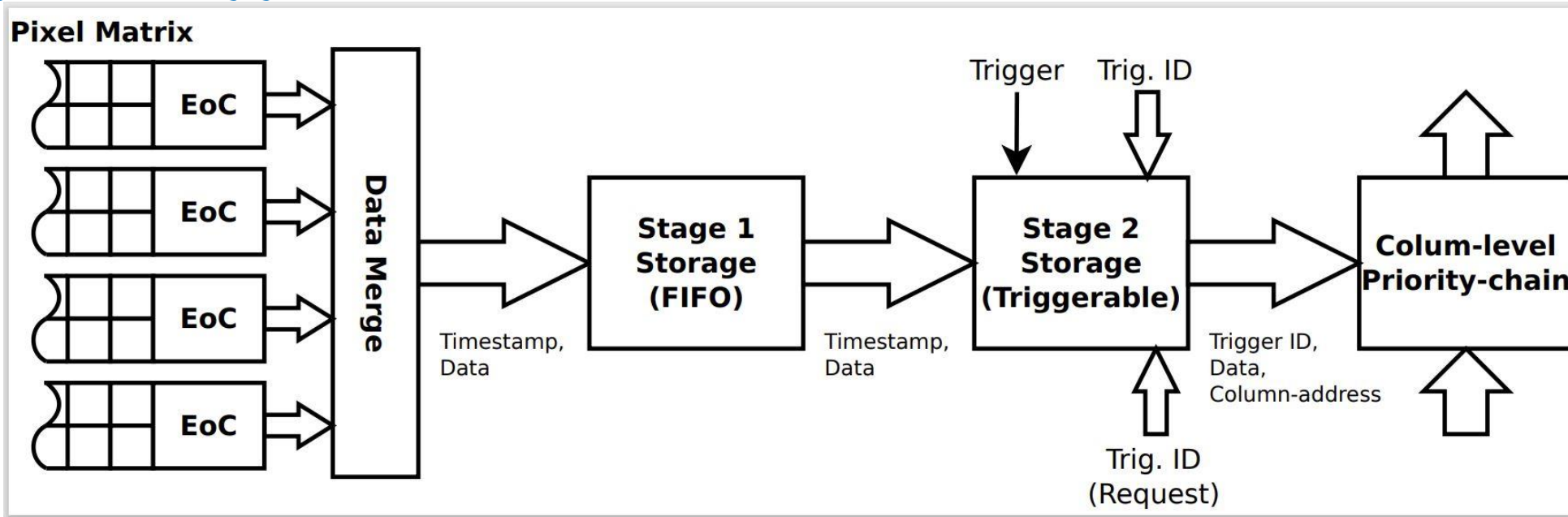


Figure 8 : Structure of Trigger Group

- New End-of-column adapted to Belle II trigger
 - - Timestamped hits stored in memories
 - - Read-out when timestamps matched with trigger
 - - spec: hit rate $\leq 120\text{MHz/cm}^2$
- Trigger memory organized in 112 Trigger Groups(TRGs), each connected to 4 DCs(EoC)
- Eoc: controls of pixel readout, extends 'Le' BCID to 9 bits
- Process the pixel data and wait for trigger commands to transmit

DCs – Double Columns
Le / Te – Leading edge / Trailing edge
BCID – Bunch Crossing ID

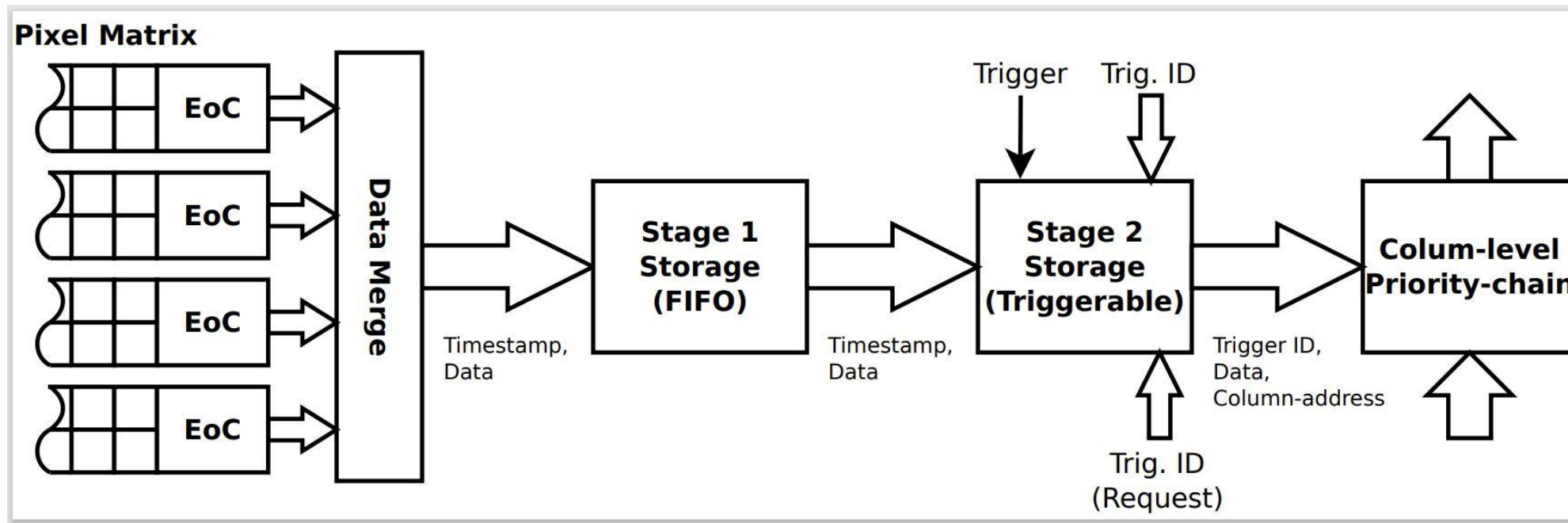


Figure 8 : Structure of Trigger Group

Data Merge:

- Collect hit data from 4DCs via 'round-robin' arbiter

Stage 1 Storage :

- Simple power friendly SRAM FIFO
- Data is buffered here until a spot in S2 is free
- Overload protection: discard data on output if it expired in S1

Stage 2 Storage :

- Data is matched to trigger
- Wait for readout after trigger
- Only works at the end of latency for each hit
- Small, more logic per data-word
- Combine pixel address + data

 


Figure 9 : Structure of Transmission Unit

- **TXU:** divider into 3 parts, general specs:
- FIFO: data buffering, transfer data_rate,
input clk 20MHz / output clk 32MHz
- Frame Generation: generate data framing necessary
- Serializer: 160MHz, output data to FPGA
- Two packages to transfer :
- command package : IDLE + SOF_C + cmd_addr + cmd + EOF_C + IDLE
- pixel data package : IDLE + SOF_H + pixel data + EOF_H + IDLE

Frame Generation: 4 data types

Pixel data – 35 bits+ 5 bits:

19-bit address – 10 bits 'row' + 3 bits 'DC' inside block + 6 bits 'block'

16-bit timing – 9 bits 'Le' BCID + 7 bits 'Te' BCID

5 bits for selecting – each frame 1 select bit + 7 data bits

CMD data: 8-bit cmd_addr + 16-bit RdReg cmd

Keywords pattern : SOF CMD/HIT, EOF CMD/HIT

IDLE pattern : K28_1 IDLE

 
 


Figure 10 : A pair of clocks with same freq and opposite phase

- Serializer : clk 160 MHz, but a data_rate of 320Mb/s is required
- Input – 10-bit parallel data,
- Baud – $32 * 10\text{Mbps}$ – 5 clk cycles for 1 data
- Output – serial data stream,
- Baud – $1 * 160\text{Mbps}$ – using 2 edges as trigger signals, increase to 320Mbps

Solution :

1. generate inverse clock – clk_n, for using both 2 rising edges
2. Separate 10-bit data into 2 groups – odd (1,3,5,7,9) & even (0,2,4,6,8)
3. 'clk' for outputting even group, 'clk_n' for outputting odd group
4. Combine the 2 outputs to achieve 320Mbps

difficulty:

1. Ensure 'clk' & 'clk_n' to be fully synchronized – tolerance 20% clk cycle
2. How to combine the 2 outputs without 320MHz clk – use both 2-level of clk for output – simulation passed

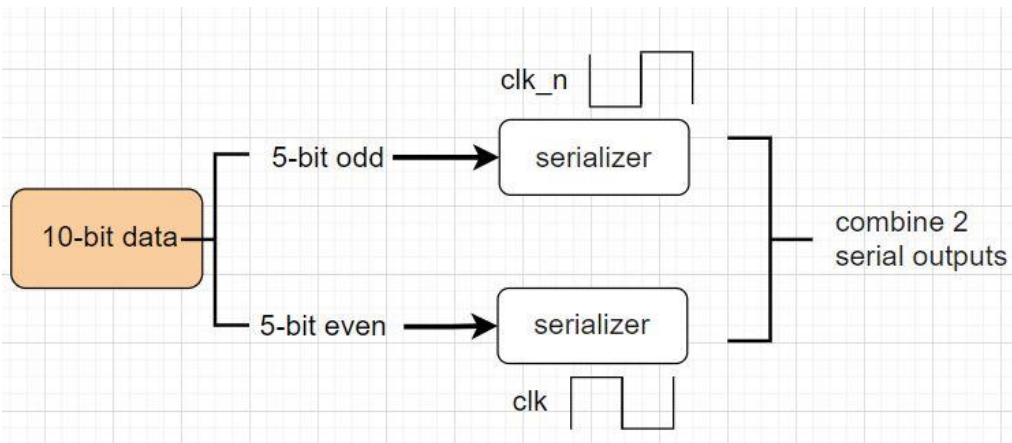


Figure 11 : conception of serializer

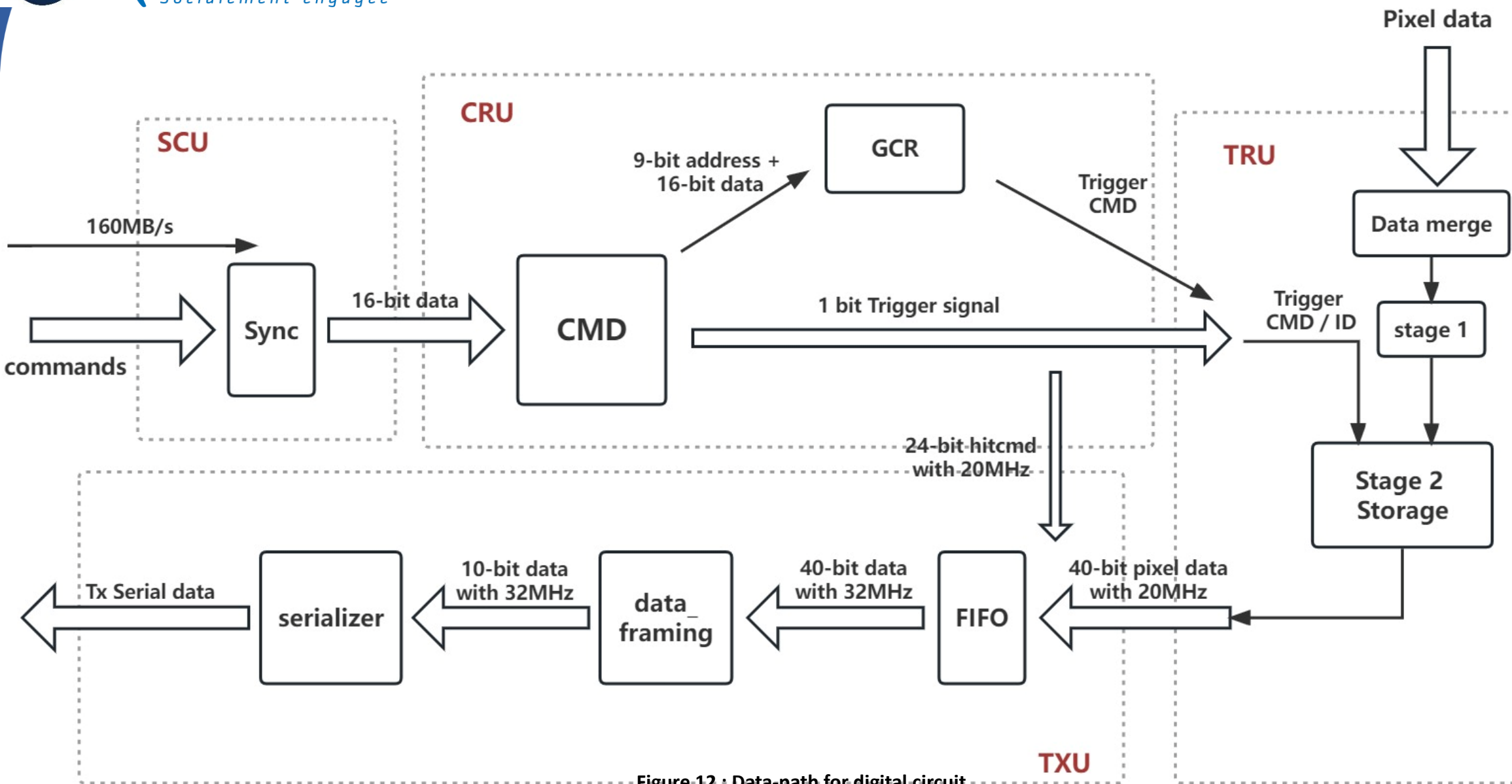


Figure 12 : Data-path for digital circuit

OBELIX_V1 : Digital Clock Path

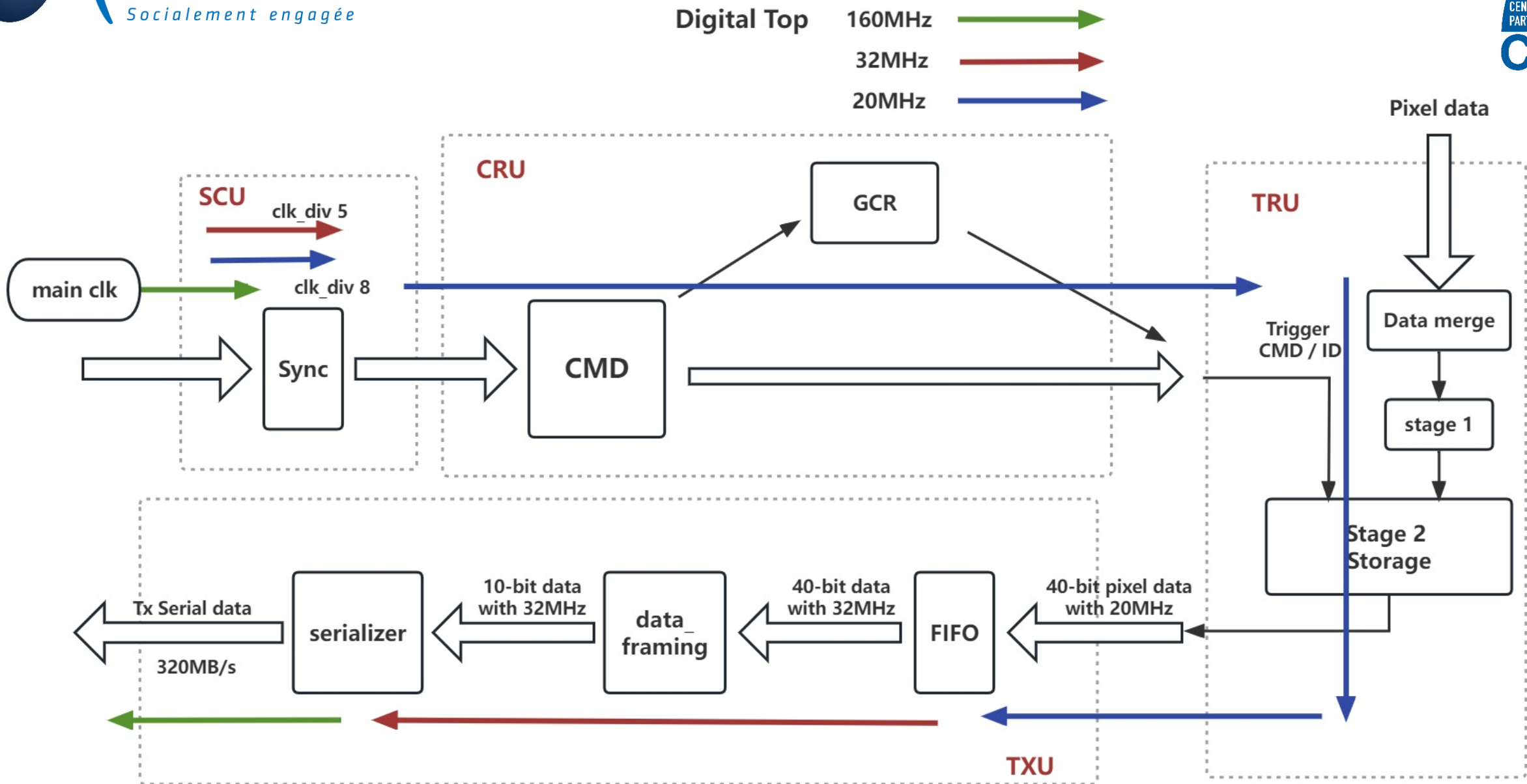


Figure 13 : Clock-path for digital circuit


Current progress and what to do next?

1. Finish the design --- all the RTL design
 - Register configurations;
 - Top level Integration
2. Back-end flows for digital top -- write scripts, almost automatically done by the EDA tool
 - synthesis global
 - Placement & Routage
 - Static Timing Analysis
 - Design Rule Checking / Layout Versus Schematic
 - Logic Equivalence Checking
 - Verification & Post simulation



Digital design – an iterative process

Back up slides

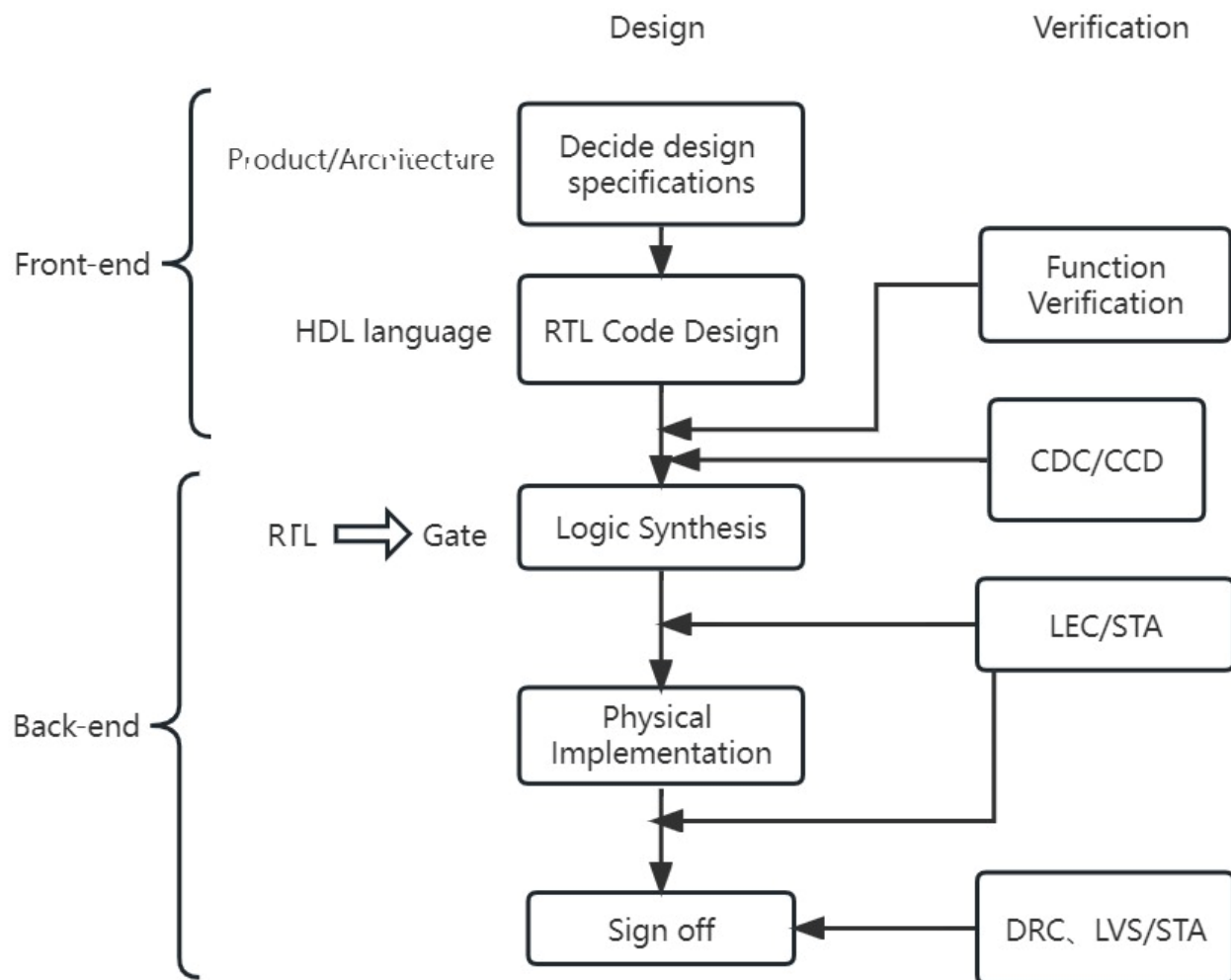

- General ASIC design flow
- **Ensure design specifications**
- **RTL Code Design** : SystemVerilog, Verilog, VHDL, etc
- **Logic synthesis**: Convert logic circuits to gate-level circuits, Genus
- **Placement & Routage**: Convert ideal circuits into real production circuit designs, Innovus
- **Signoff**
- General ASIC verification flow
- **Logical verification**: simulation, xcelium / questa
- **CCD/CDC**: constraint check for syn , clock domain check for rtl
- **Static Timing Analysis** : check timing violation, tempus
- **LEC check**: verify design consistency, conformal
- **DRC, LVS**: design rule check & layout versus schematic, Innovus
- **Verification**: post-simulation, verification, UVM

Figure 14 : General design flow for ASIC design

OBELIX_V1 : Digital Clock Path

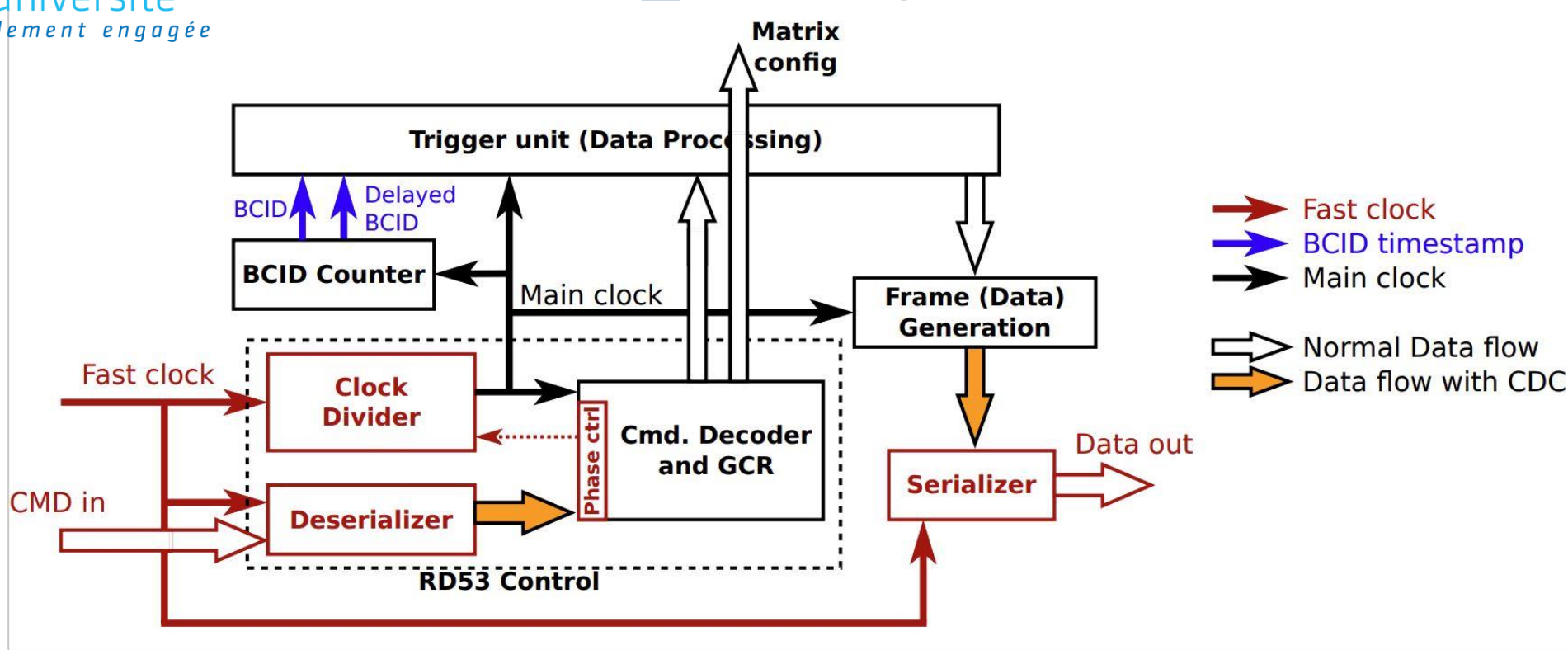


Figure 15 : Clock domain of Obelix digital top

Clock Signal	Ideal	Alignment RF Clk
Main Clock	160MHz	169.7MHz
Divider 8 Clock	20 MHz	21.2 MHz
BCID Clock	20 MHz	21.2 MHz
TXU Clock	32MHz	33.9MHz

Table 1 : CLK frequency for digital design and RF clk

Thanks for your attention