

Simulation model for discharges study in MPGD

Meeting SPLAM 03/02/2012


Simulation model for discharges study in MPGD (μ megas)

GOAL :

- Define the optimum material for the resistive layer and the optimum size and thickness (spark protection/signal collection)


BUT : model must be correct in order to have a good background

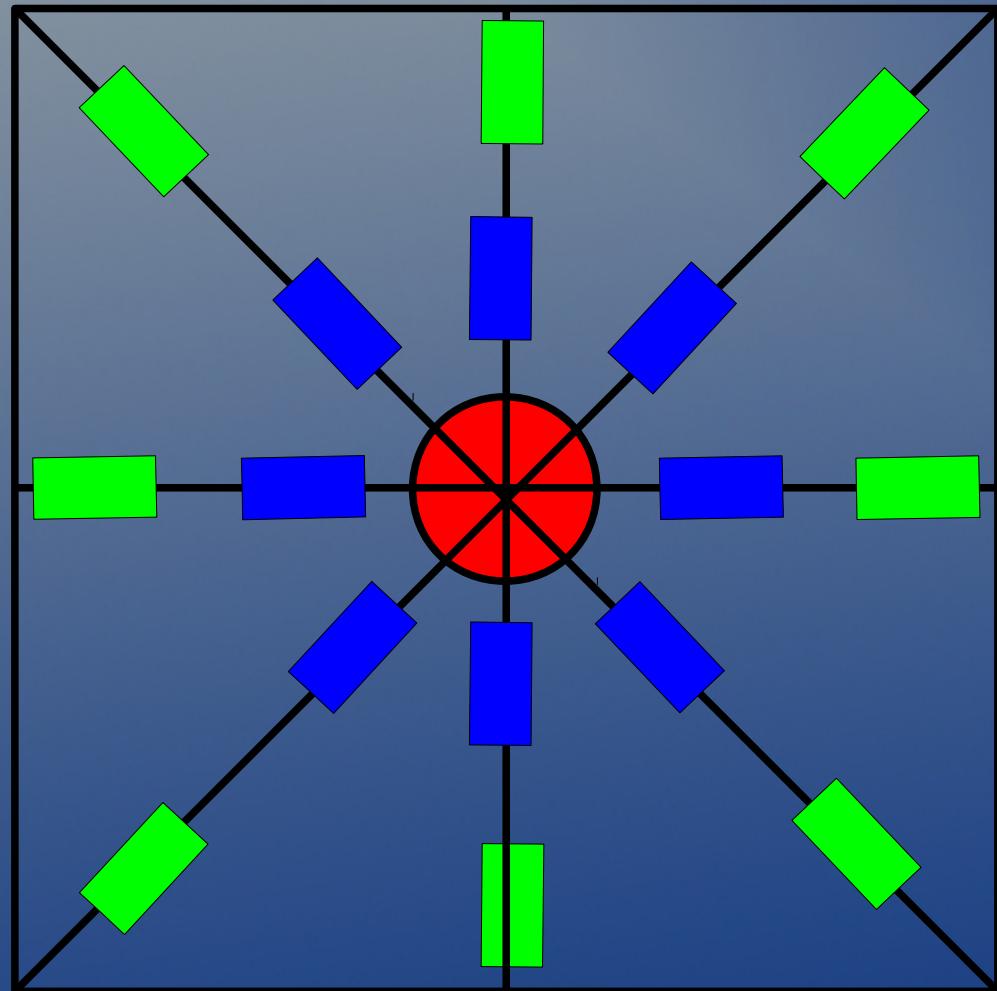Simulation model for discharges study in MPGD (μ megas)




Modelisation of the mesh and the ground plane : connection with the neighbour via resistor ($R = 10 \text{ m}\Omega$ for horizontal and vertical and $14 \text{ m}\Omega$ for diagonal) and inductance ($L = 100 \text{ fH}$)
The pad and mesh described by a point

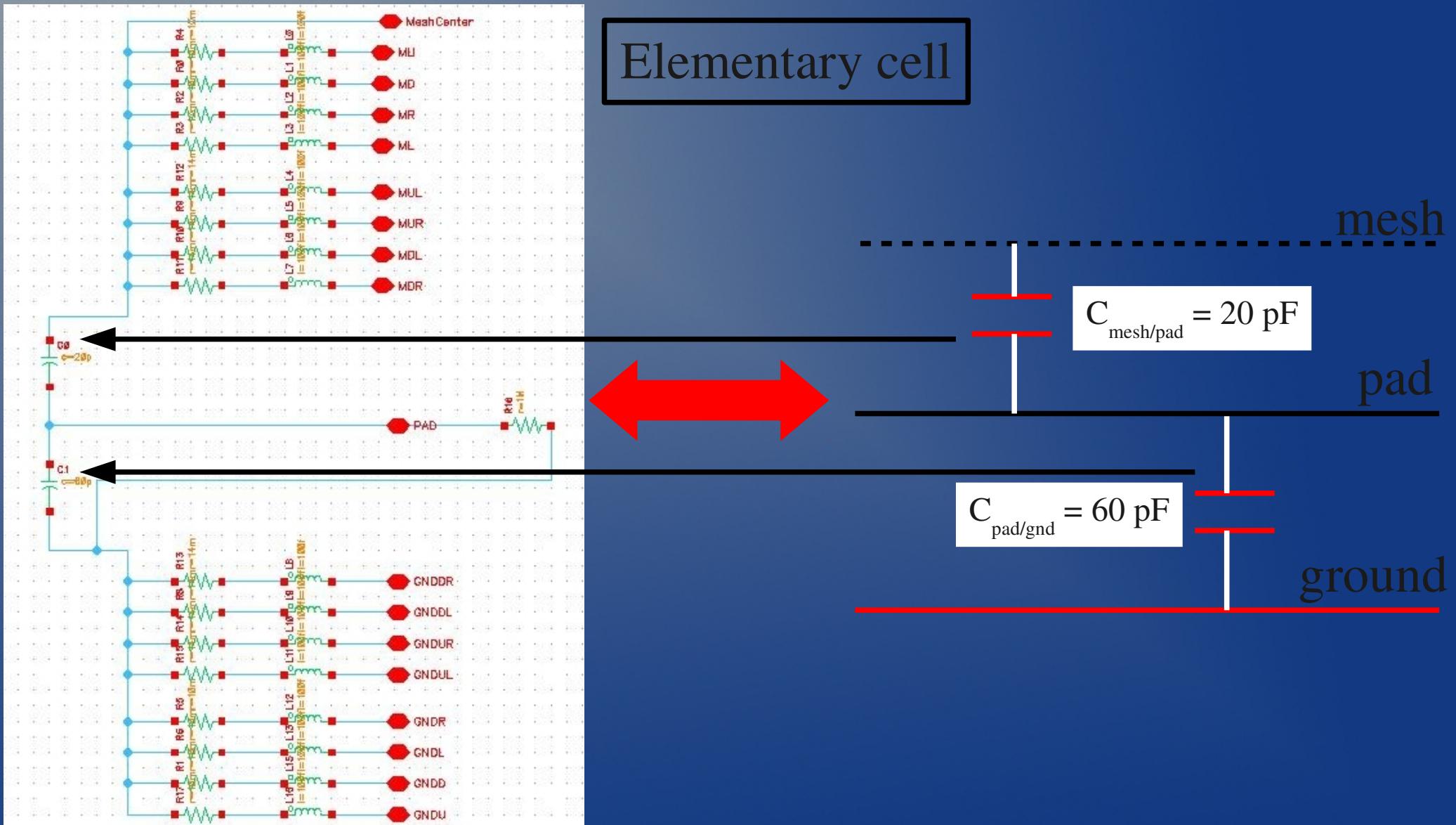Simulation model for discharges study in MPGD (μ megas)



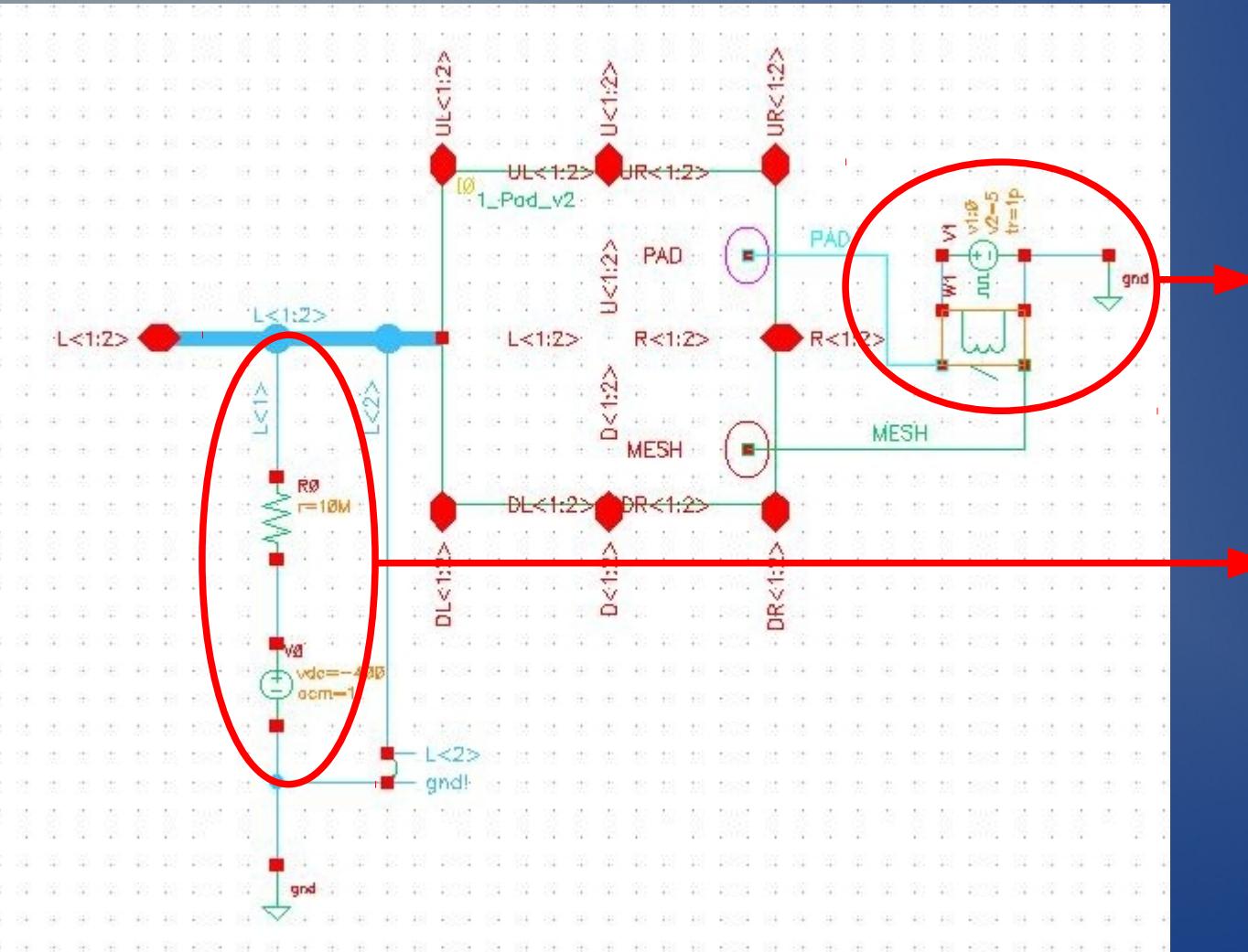
Simulation model for discharges study in MPGD (μ megas)



Switch to modelise
discharge (short cut
between mesh and pad)

Power supply of the mesh

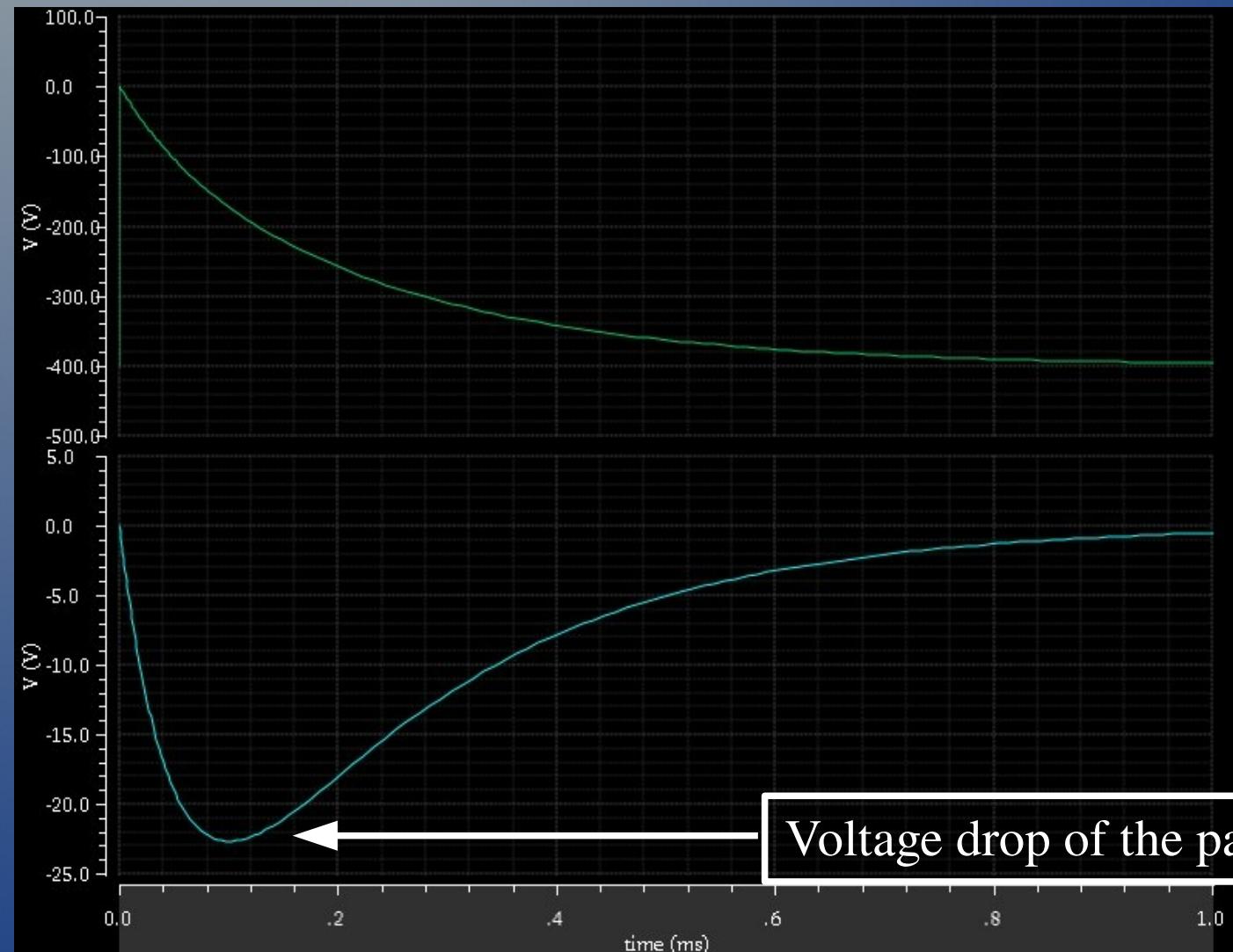
Simulation model for discharges study in MPGD (μ megas)



Discharge model:
switch closed @ 1μ s
rise time = fall time = 1 ps
pulse duration = 1 ns

Fast component for the
mesh and slow for the pad

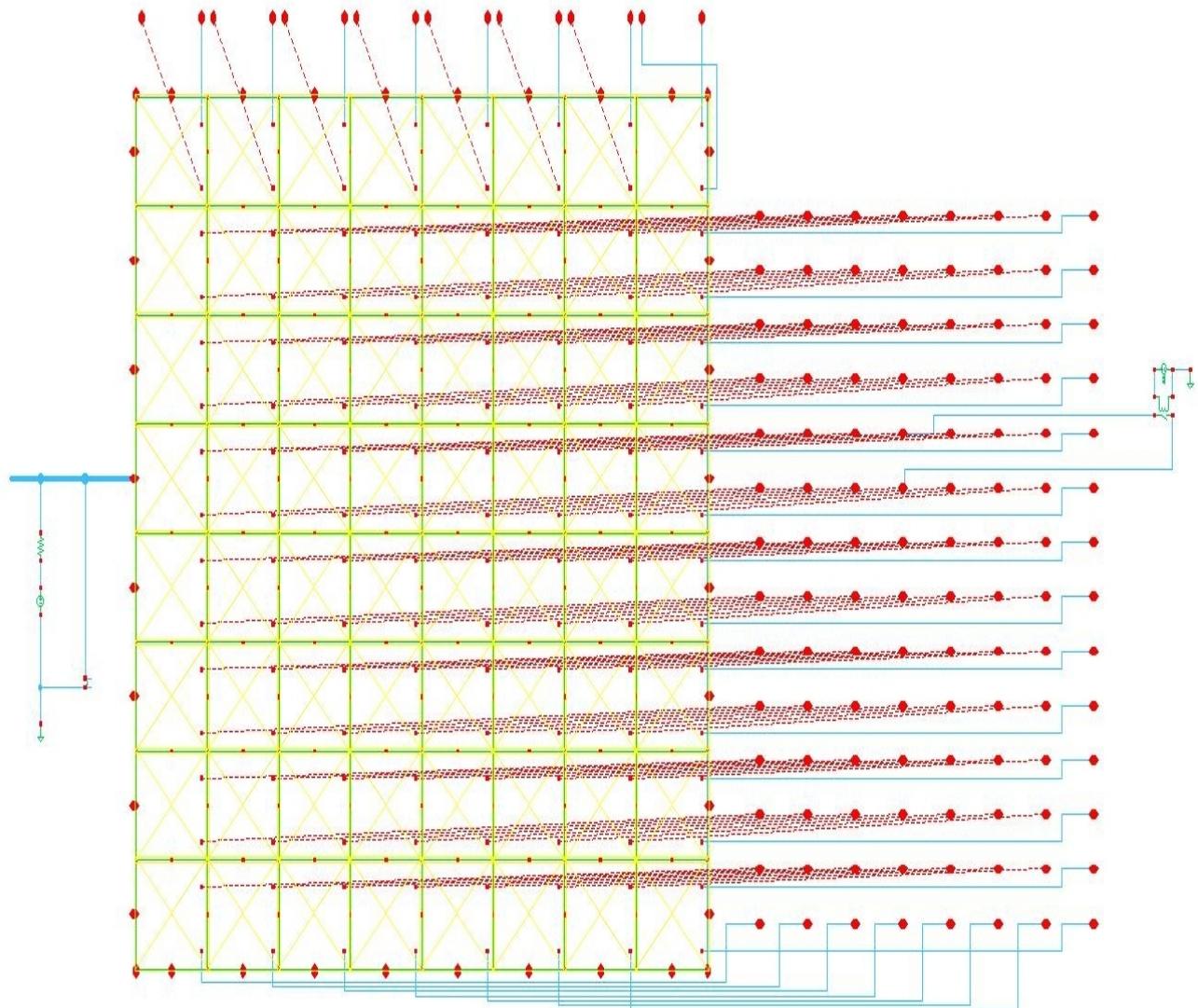
Simulation model for discharges study in MPGD (μ megas)




64 pads model
=> extend the model
to $N \times N$ pads

Simulation model for discharges study in MPGD (μ megas)

Discharge propagation over a 8×8 cell

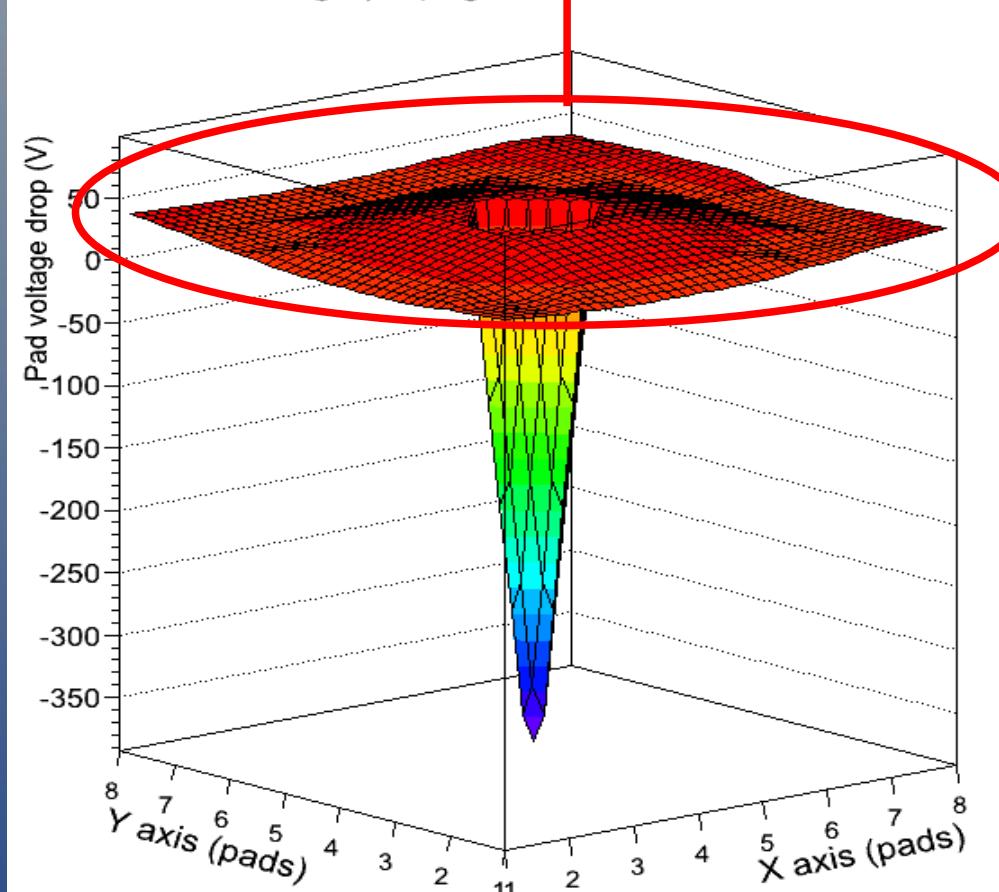

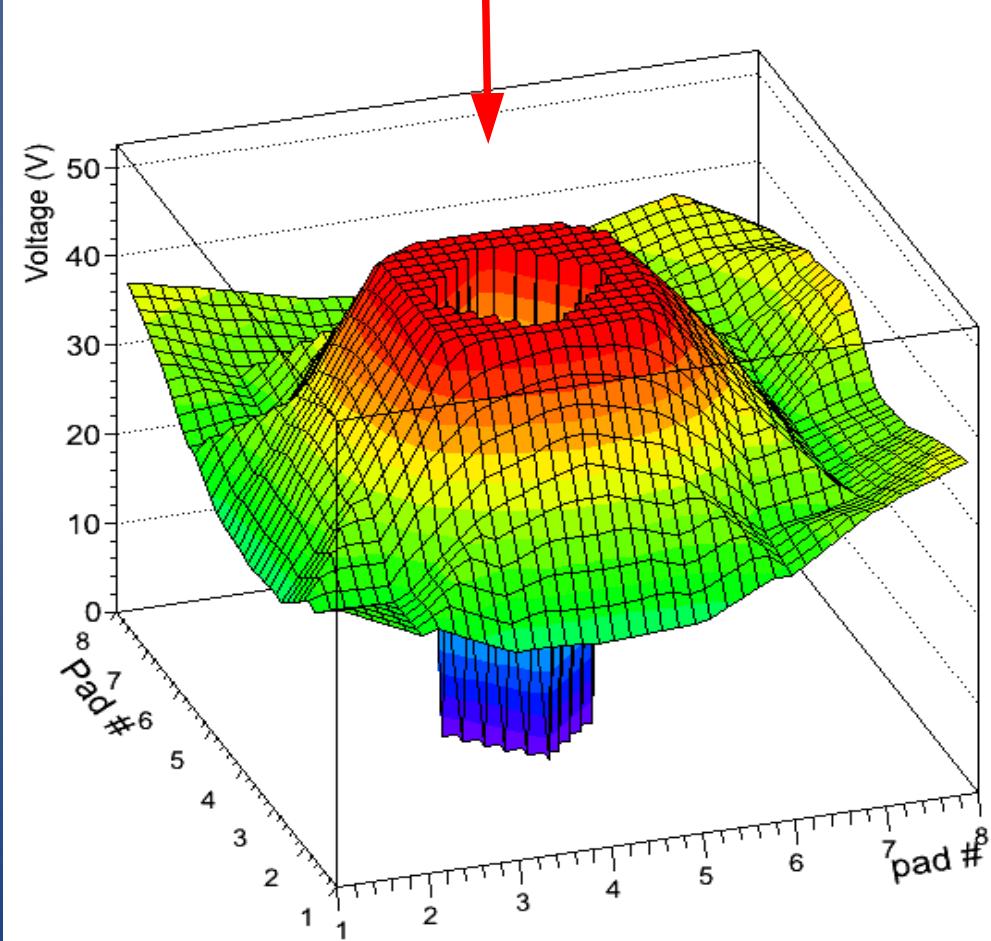
Discharge propagation over an ASU (zoom for positive values)



Discharge pad voltage \rightarrow mesh voltage (-400V)

Neighbors pads compensate with positive voltage

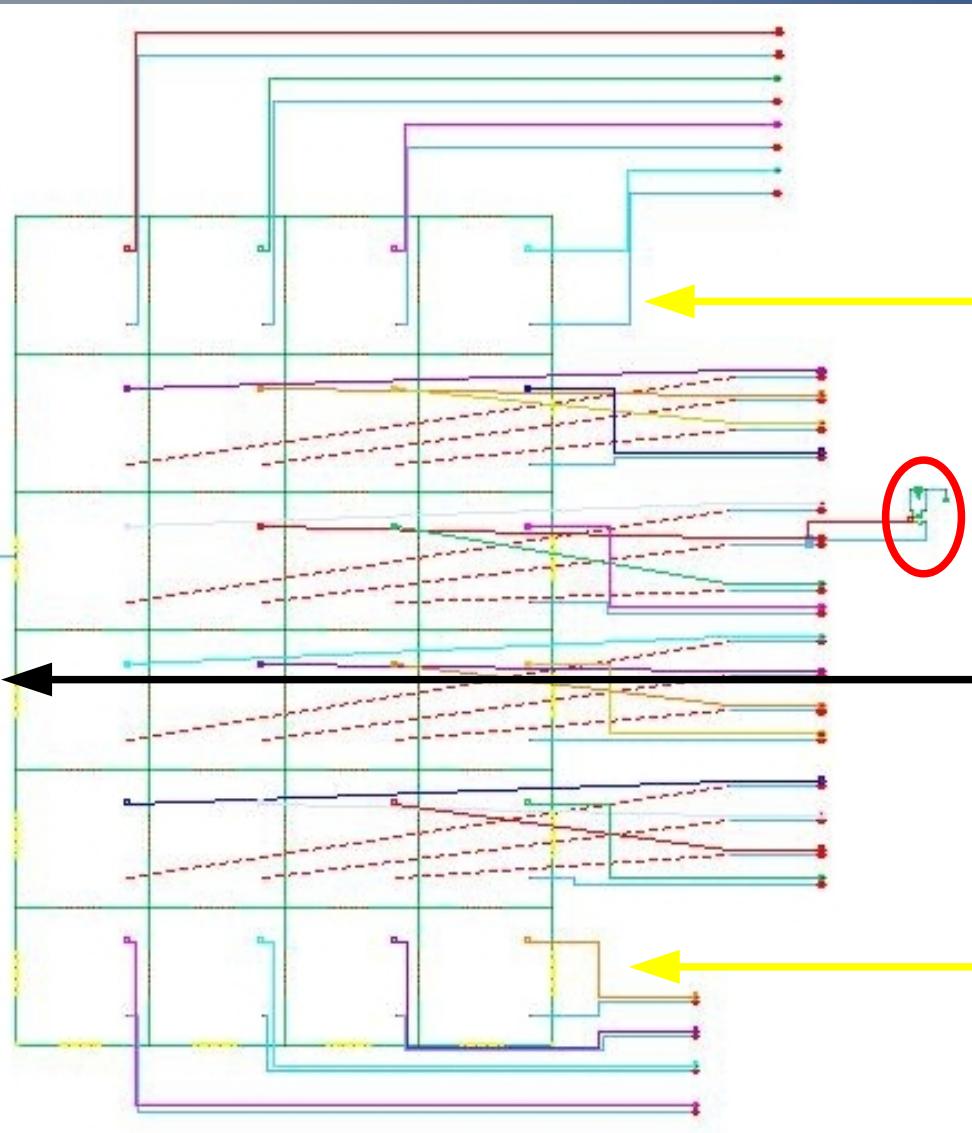Simulation model for discharges study in MPGD (μ megas)



32×48 pads model
using 8×8 cells

Bus of 64 meshes


Switch

Power supply of the mesh


Bus of 64 pads

Simulation model for discharges study in MPGD (μ megas)

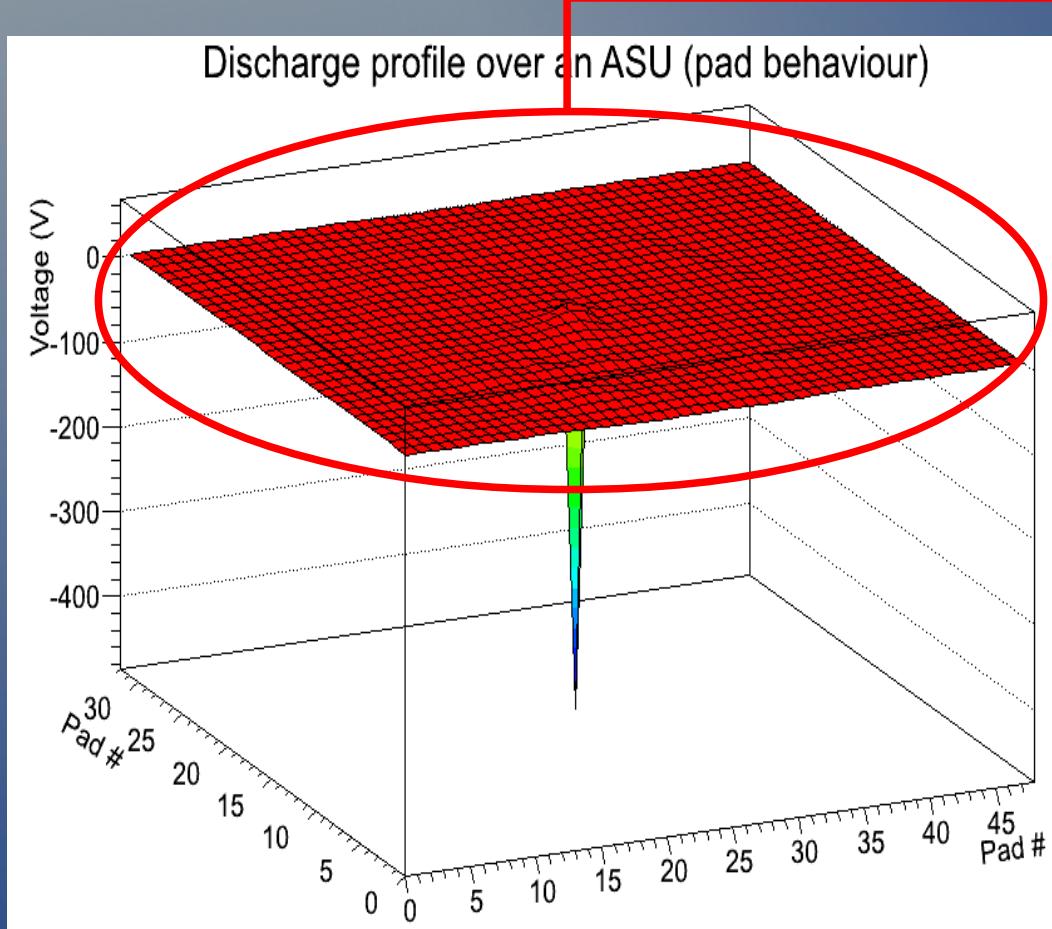Discharge profile over an ASU (pad behaviour)



Discharge profile over an ASU

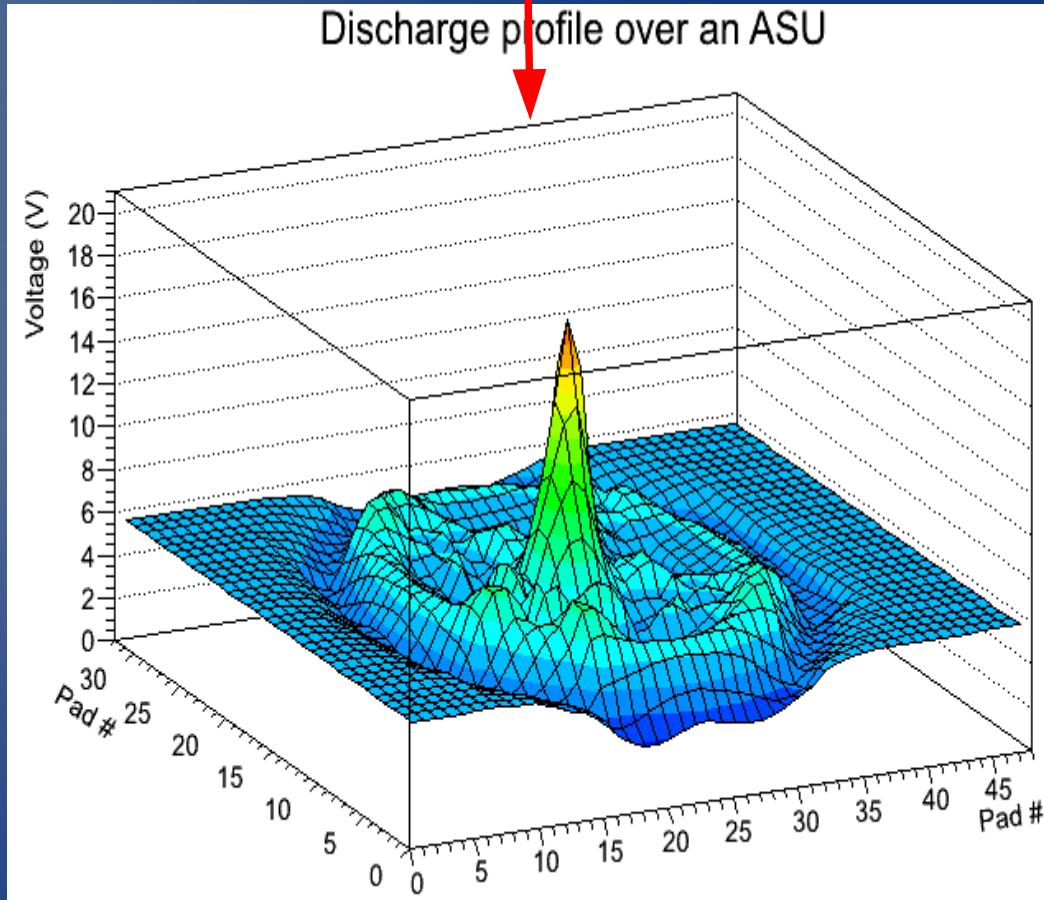

Same behavior as with 64 pads but lower voltage drop due to greater # of pads

Summary and future work

1. Implement resistive material in the simulations and observe the effect
2. Perform measurements with a dedicated electronic pcb and compare results with simulations
3. Improve the model → more accurate simulations to determine the optimum value for the resistive layer