

# DC-DC Conversion Powering Schemes for the CMS Tracker Upgrade

Katja Klein, RWTH Aachen University

with L. Feld, W. Karpinski, J. Merz, J. Sammet, O. Scheibling, A. Schultz von Dratzig, M. Wlochal

International Europhysics Conference on High-Energy Physics, Grenoble, 21. - 27. 7. 2011



## Power provision for the CMS tracker



Today, the CMS strip tracker needs 33kW; CMS pixel detector needs 3.8kW

→ Power consumption will increase for SLHC: more readout channels, additional functionality...



50m long cables → 50% Ohmic losses, too much material



Services nested with others and cable channels full


Novel powering schemes have to be exploited for the CMS strip tracker and pixel detector upgrades

## A DC-DC conversion powering scheme

Idea: deliver detector power at higher voltage and lower current  
 $P = U \times I = (rU) \times (I/r)$   
 $r = \text{conversion ratio} \sim 5-10$

→ Ohmic power losses in supply cables are reduced by factor  $1/r^2$   
 → Motherboards and cables can be thinner → less material

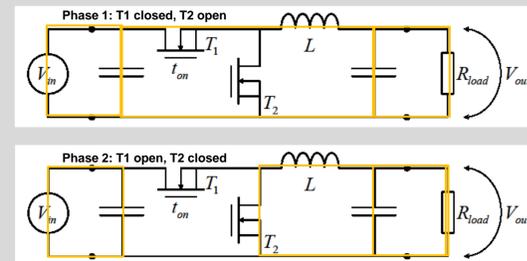
DC-DC buck converters used to convert  $rU$  back to required voltage  $U$



Challenges: radiation hardness of high voltage power transistors (CERN), switching noise, magnetic emissions, material budget

## DC-DC buck converters for CMS

"PIX\_V7":

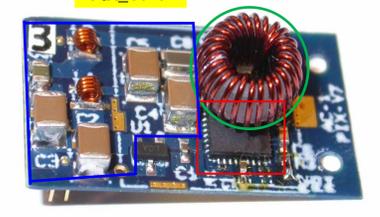

ASIC: AMIS2 by CERN  
 $I_{out} < 3A$   
 $V_{in} < 12V$   
 $f_s$  configurable, e.g. 1.3MHz

PCB:  
 2 copper layers a 35µm  
 0.3mm thick  
 Large ground area on back for cooling

Toroidal inductor:  
 $L = 450nH$   
 $R_{DC} = 40m\Omega$   
 Plastic core

PI-filters at in- and output

Shield  
 Shielding of magnetic field;  
 reduction of conductive noise through segregation;  
 cooling contact


$A = 28 \times 16 \text{ mm}^2$   
 $M \approx 2.5g$   
 3.8% of a radiation length

Integration onto supply tube  
 ✓ Pseudorapidity  $\eta \sim 4$   
 ✓ Large distance to pixel modules  
 ✓ Sufficient space  
 ✓ CO<sub>2</sub> cooling

- 1 DC-DC converter powers 1-4 pixel modules
- Output current per converter < 3A
- $V_{in} = 12V$
- $V_{out} = 2.5V$  and  $3.3V$

→ 2 000 DC-DC converters required for pixel upgrade (~ 2016)
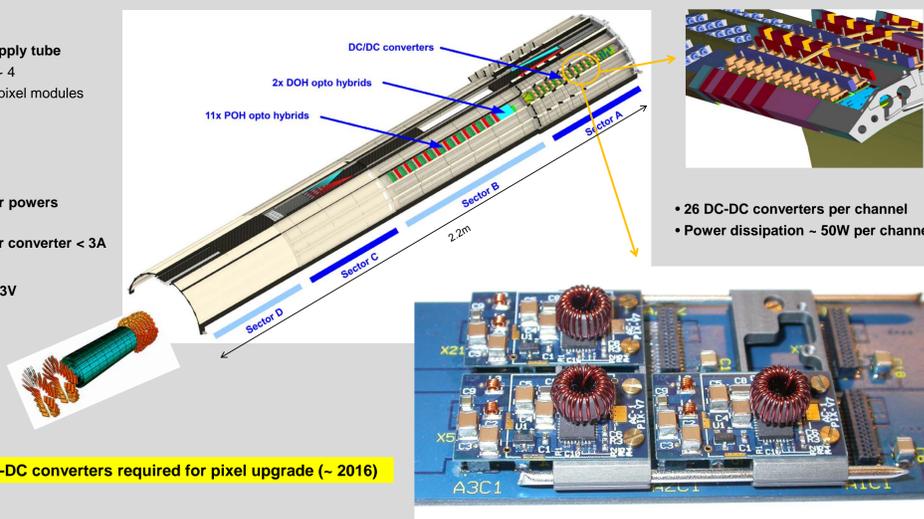
## Integration into the future CMS pixel system



- 26 DC-DC converters per channel
- Power dissipation ~ 50W per channel


## Power efficiency

• Phase 1 conditions:  
 $V_{out} = 3.3V$  or  $2.5V$ ,  $I_{out} < 2.8A$ ,  
 conversion ratio of 3-4  
 → 75% - 80% efficiency


→ Efficiency sufficient for phase-1

• Phase 2 conditions:  
 $V_{out} = 1.25V$ ,  $I_{out} = 3A$ ,  
 conversion ratio of 8-10  
 → about 55% efficiency

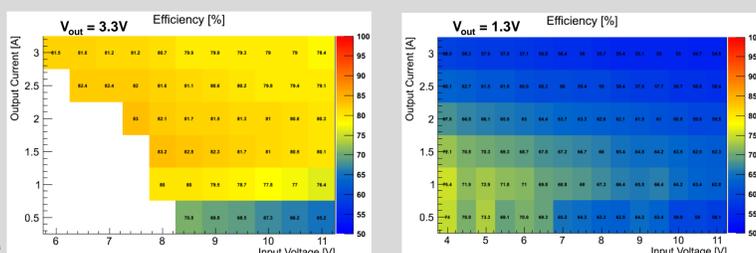Possible solution for phase-2:  
 combination with an on-chip "switched capacitor"  
 converter with  $r = 2$




## Conductive noise emissions

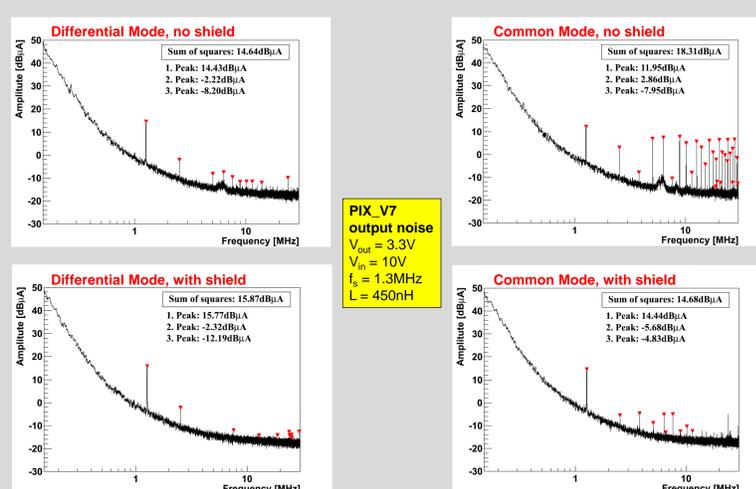


PIX\_V7 output noise  
 $V_{out} = 3.3V$   
 $V_{in} = 10V$   
 $f_s = 1.3MHz$   
 $L = 450nH$

→ Conductive noise emissions are low  
 → Shield reduces high-frequency components (segregation between noisy and quiet parts of PCB)



## Shielding of the magnetic field

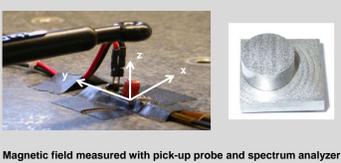

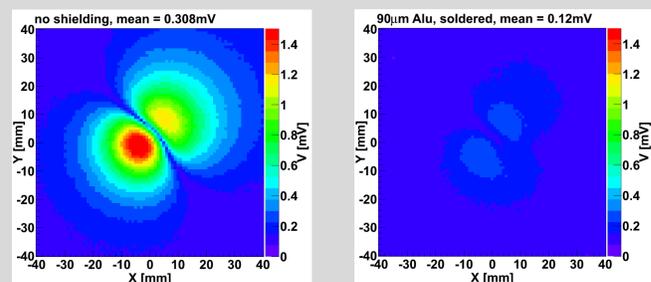
→ Shielding with 90µm thick Aluminium cap is sufficient






## Cooling performance

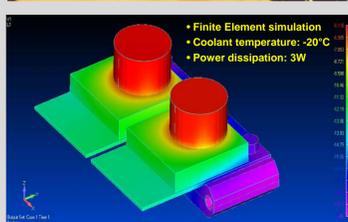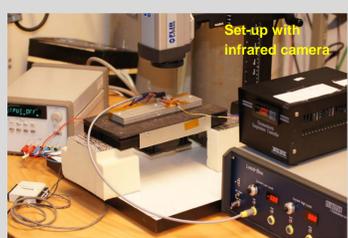

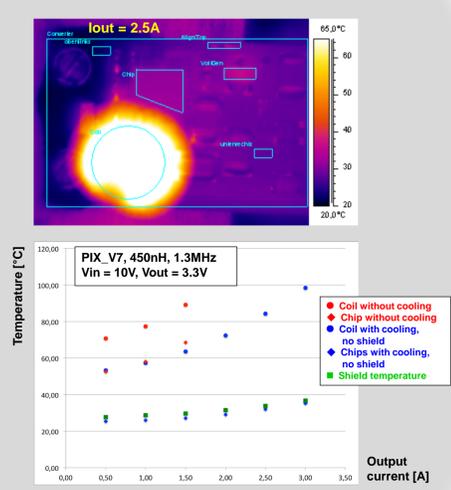→ Measurements with infrared camera and FE calculations indicate  $\Delta T$  of ~ 15K to coolant temperature



## Pixel module noise

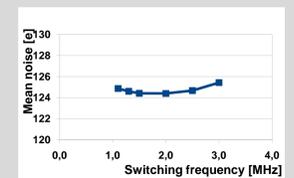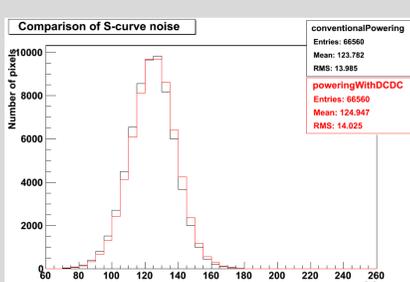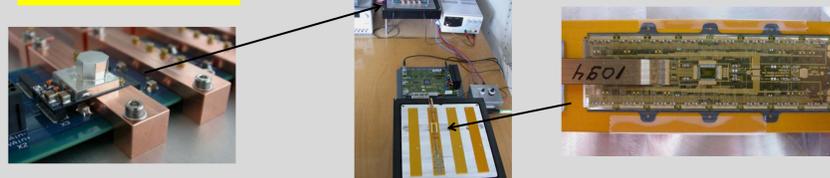

Noise of CMS pixel modules measured with and without DC-DC converter  
 → no significant increase due to DC-DC converters!

→ DC-DC buck converters with a conversion ratio of ~ 4 will be used for the CMS pixel upgrade; R&D for phase-2 is ongoing.